 

Chapter Four – I (1/4)

1

The Big Picture: The Performance Perspective

- Performance of a machine is determined by:
 - Instruction count
 - Clock cycle time
 - Clock cycles per instruction
- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction
- Single cycle processor - one clock cycle per instruction
 - Advantages: Simple design, low CPI
 - Disadvantages: Long cycle time, which is limited by the slowest instruction.




How to Design a Processor: step-by-step

1. Analyze instruction set → datapath requirements
 - the meaning of each instruction is given by register transfers
 $R[rd] \leftarrow R[rs] + R[rt];$
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
2. Select set of datapath components and establish clocking methodology
3. Design datapath to meet the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Design the control logic

CE, KWU Prof. S.W. LEE 3

Review: The MIPS Instruction Formats

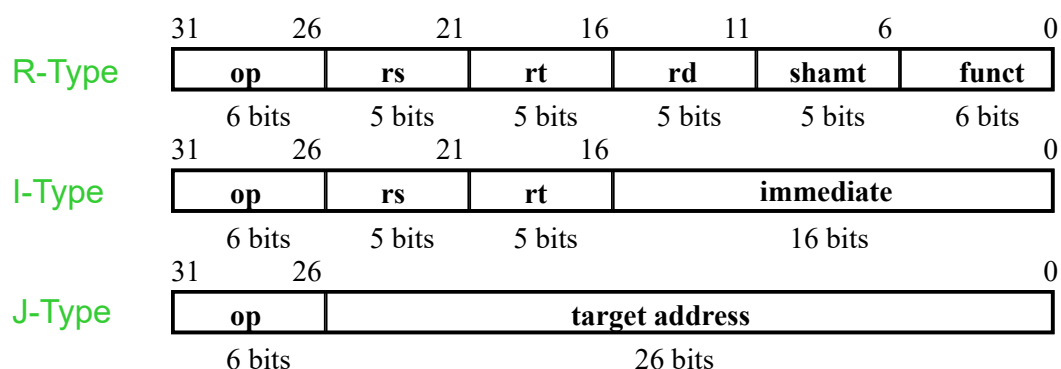- All MIPS instructions are 32 bits long. The three instruction formats are:



- The different fields are:
 - op: operation of the instruction
 - rs, rt, rd: the source and destination register specifiers
 - shamt: shift amount
 - funct: selects the variant of the operation in the “op” field
 - address / immediate: address offset or immediate value
 - target address: target address of the jump instruction

CE, KWU Prof. S.W. LEE 4

The Processor: Datapath & Control

- Designing an implementation that includes a **subset of the core MIPS** instruction set:
 - The memory-reference instructions: `lw`, `sw`
 - The arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `slt`
 - The control flow instructions: `beq`, `j`
- For every instruction except `j`, **the first two steps** are identical:
 - **Send the program counter (PC)** to the memory that contains the code and **fetch the instruction** from that memory
 - **Read one or two registers**, using fields of the instruction to select the registers to read. For the load word instruction, we need to read only one register.
- After these two steps, the actions required to complete the instruction depend on the instruction class
- All instructions use the ALU after reading the registers. Why?

CE, KWU Prof. S.W. LEE 5

Step 1a: The MIPS Subset

- **R-Type**

31	26	21	16	11	6	0
op	rs	rt	rd	shamt	funct	
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	

 - **ADD and SUB**
 - `addu rd, rs, rt`
 - `subu rd, rs, rt`
- **I-Type**

31	26	21	16	0
op	rs	rt	immediate	
6 bits	5 bits	5 bits	16 bits	

 - **OR Immediate:**
 - `ori rt, rs, imm16`
 - **LOAD and STORE**
 - `lw rt, imm16(rs)`
 - `sw rt, imm16(rs)`
 - **BRANCH:**
 - `beq rs, rt, imm16`

CE, KWU Prof. S.W. LEE 6

Register Transfer Logic (RTL)

- RTL gives the **meaning** of the instructions
- All instructions start by fetching the instruction

op		rs		rt		rd		shamt		funct	=	MEM[PC]
op		rs		rt		Imm16					=	MEM[PC]

inst Register Transfers

addu	R[rd]	←	R[rs] + R[rt];	PC	←	PC + 4
subu	R[rd]	←	R[rs] - R[rt];	PC	←	PC + 4
ori	R[rt]	←	R[rs] zero_ext(imm16);	PC	←	PC + 4
load	R[rt]	←	MEM[R[rs] + sign_ext(imm16)];	PC	←	PC + 4
store	MEM[R[rs] + sign_ext(imm16)] ← R[rt];			PC	←	PC + 4
beq	if (R[rs]==R[rt])					
			then PC ← PC + 4 + (sign_ext(imm16)<<2)			
			else PC ← PC + 4			

CE, KWU Prof. S.W. LEE 7


Step 1: Requirements of the Instruction Set

- Memory
 - instruction & data
- Registers (32 x 32)
 - read rs
 - read rt
 - write rt or rd
- PC
- Extender (sign extend or zero extend)
- Add and sub register or extended immediate
- Add 4 or shifted extended immediate to PC

CE, KWU Prof. S.W. LEE 8

More Implementation Details

- **Abstract / Simplified View:**

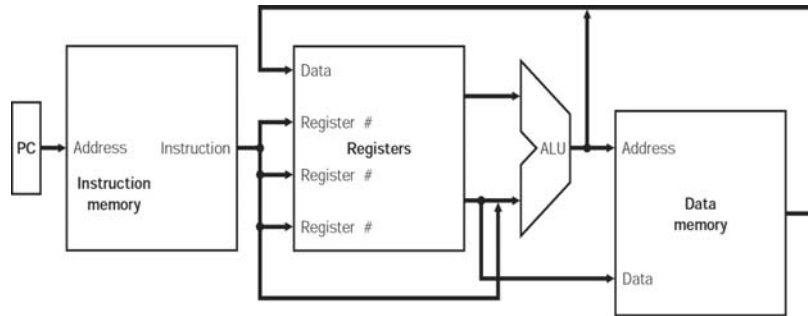

- **The functional units in the MIPS implementation consist of two different types of logic elements:**
 - **Elements that operate on data values (combinational)**
 - Outputs depend only on the current inputs.
 - **Elements that contain state (sequential)**
 - They have internal storage.
 - At least two inputs (clock and data) and one output (data)
 - E.g. D flip-flop

CE, KWU Prof. S.W. LEE 9


Step 2: Components of the Datapath

- **Combinational Elements: Does not use a clock**


- **AND-gate**
 - $Y = A \& B$




- **Adder**
 - $Y = A + B$

 

- **Multiplexer**
 - $Y = S ? I1 : I0$

 

 - **Arithmetic/Logic Unit**
 - $Y = f(A, B)$



CE, KWU Prof. S.W. LEE 10




Sequential Element

- **Register (Basic Building Blocks)**

- **Edge-triggered:** update when Clk changes from 0 to 1
- **Similar to the D Flip Flop except**
 - N-bit input and output
 - Write enable input

- **Write Enable:**

   - negated (0): Data Out will not change
- asserted (1): Data Out will become Data In on the falling edge of the clock



CE, KWU Prof. S.W. LEE

11

Storage Element: Register File

- **Register File consists of 32 registers:**


- Two 32-bit output busses: busA and busB
- One 32-bit input bus: busW

- **Register is selected by:**

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- **Clock input (CLK)**

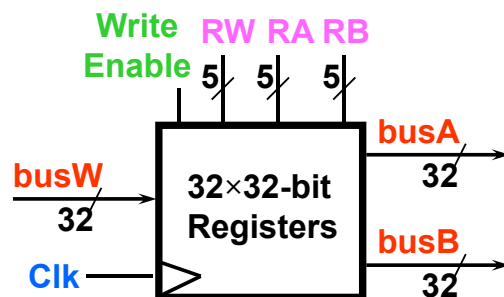- The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid => busA or busB valid after “access time.”




CE, KWU Prof. S.W. LEE

12


Storage Element: Idealized Memory

- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is selected by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - The CLK input is a factor **ONLY** during write operation
 - During read operation, memory behaves as a combinational logic block:
 - Address valid => Data Out valid after “access time.”

 

CE, KWU Prof. S.W. LEE 13

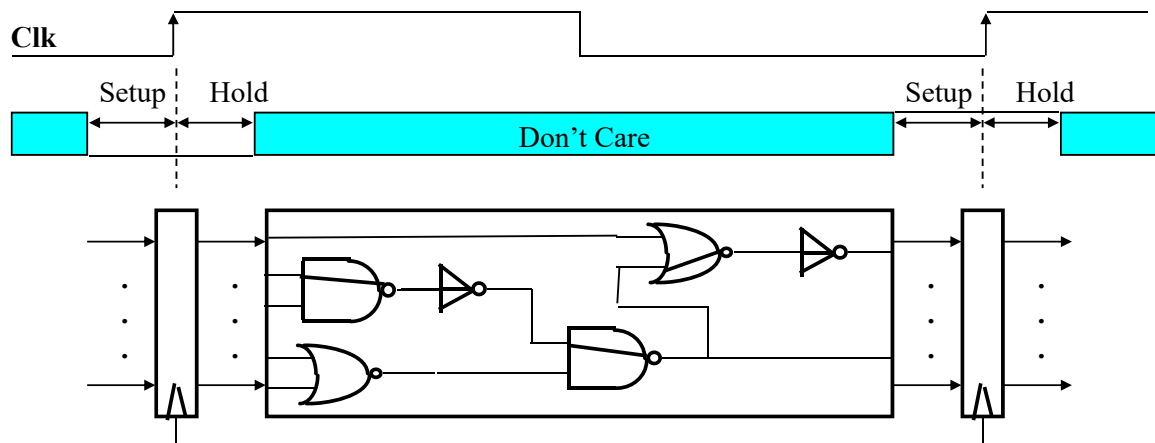
Clocking Methodology – Positive Edge Triggered



- All storage elements are clocked by the same clock edge
- Cycle Time = CLK-to-Q + Longest Delay Path + Setup + Clock Skew
- (CLK-to-Q + Shortest Delay Path – Clock Skew) > Hold Time

CE, KWU Prof. S.W. LEE 14

Combinational vs. Sequential

 

- **Combinational logic, state elements, and the clock**
 - Any inputs to a state elements must reach a stable value before the active clock edge causes the state to be updated.
 - The time necessary for the signals to travel from SE1 to SE2 defines the clock cycle length
- **Allows a state element to be read and written in the same clock cycle without causing a race condition.**

CE, KWU Prof. S.W. LEE

15

Step 3: Design Datapath


- **Register Transfer Requirements → Datapath Design**
 - Instruction Fetch
 - Decode instructions and Read Operands
 - Execute Operation
 - Write back the result

CE, KWU Prof. S.W. LEE

16

Datapath for Instruction Fetch

 - The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{"something else"}$




- PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- Reading from the Instruction Memory is a combinational activity, so it doesn't need an explicit read control signal

CE, KWU Prof. S.W. LEE 17

Decoding Instructions

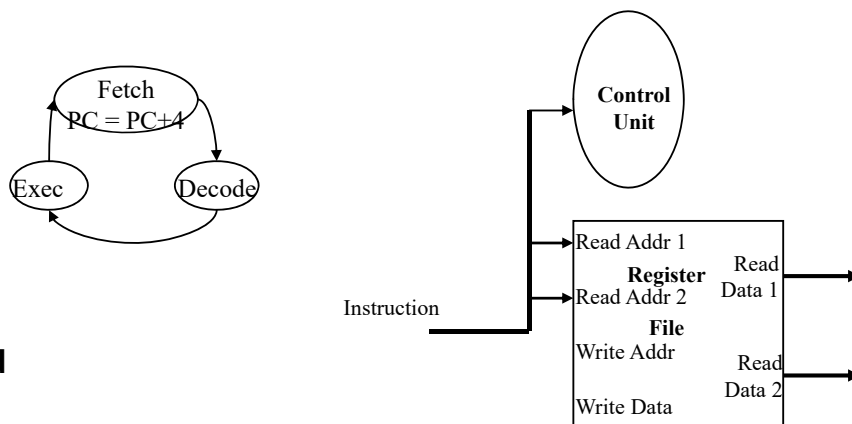- Decoding instructions involves
 - sending the fetched instruction's opcode and function field bits to the control unit





– And

- Reading two values from the Register File
 - Register File addresses are contained in the instruction

CE, KWU Prof. S.W. LEE 18

Datapath for R-type ALU operations



- Register file and ALU

 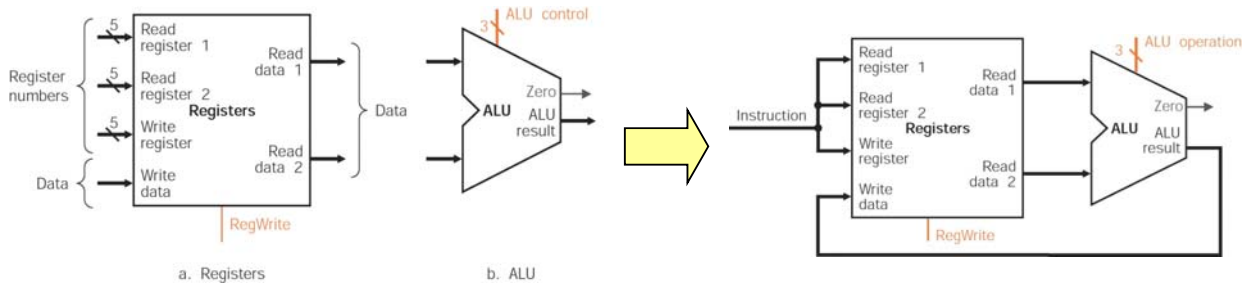

CE, KWU Prof. S.W. LEE 19

Datapath for Add & Subtract

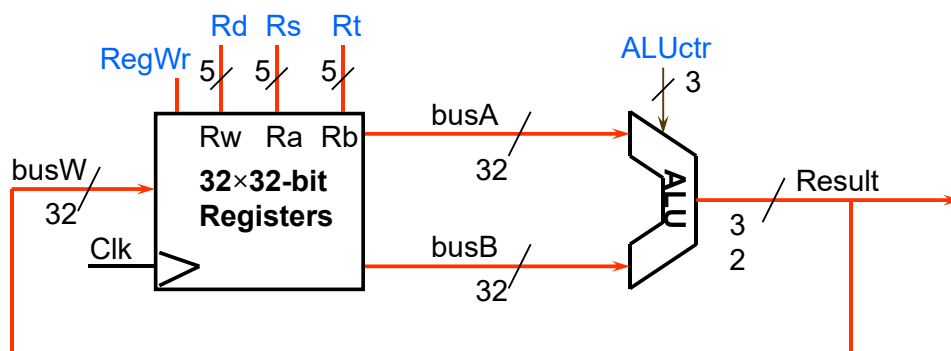 
- $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: `addu rd, rs, rt`
 - R_a , R_b , and R_w come from instruction's `rs`, `rt`, and `rd` fields
 - `ALUctr` and `RegWr`: control logic after decoding the instruction



- Note that Register File is not written every cycle (e.g. `sw`), so we need an explicit write control signal for the Register File


CE, KWU Prof. S.W. LEE 20

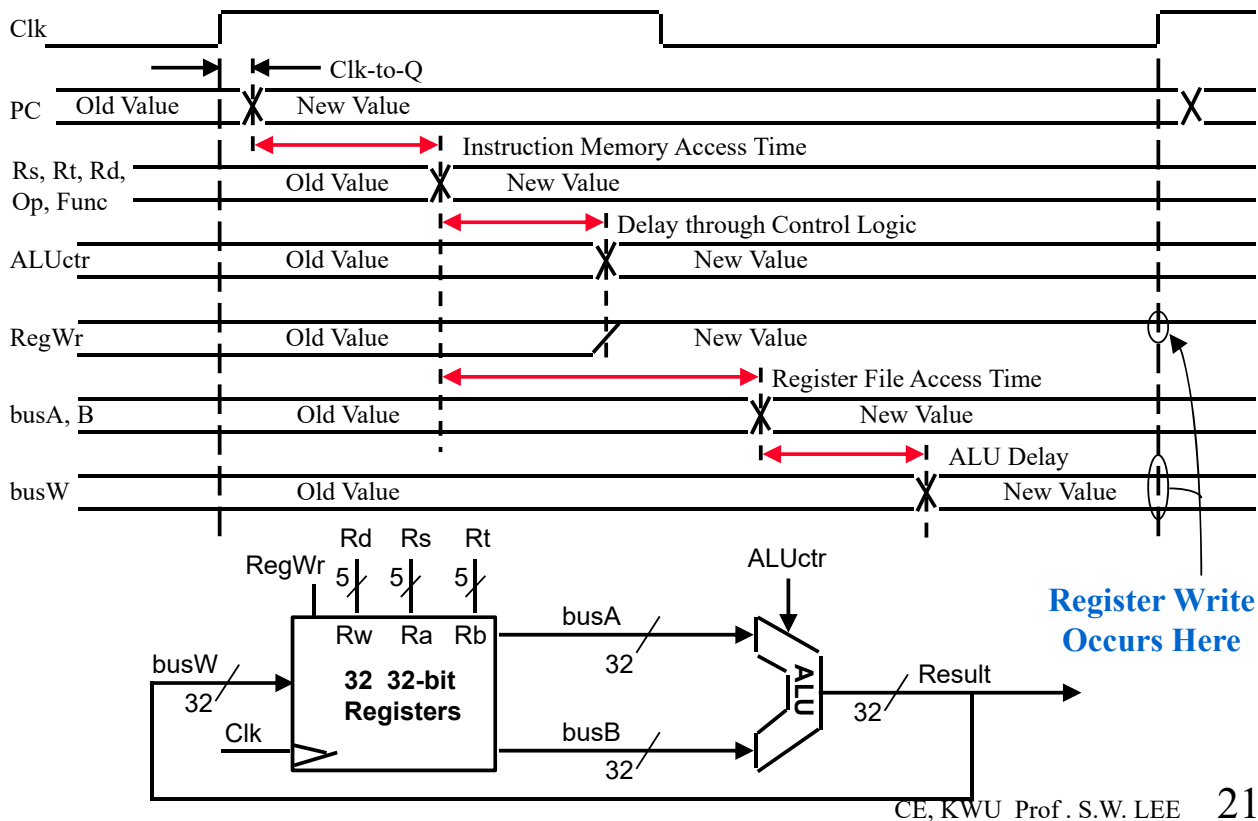Register-Register Timing: One complete cycle





Logical Operations with Immediate

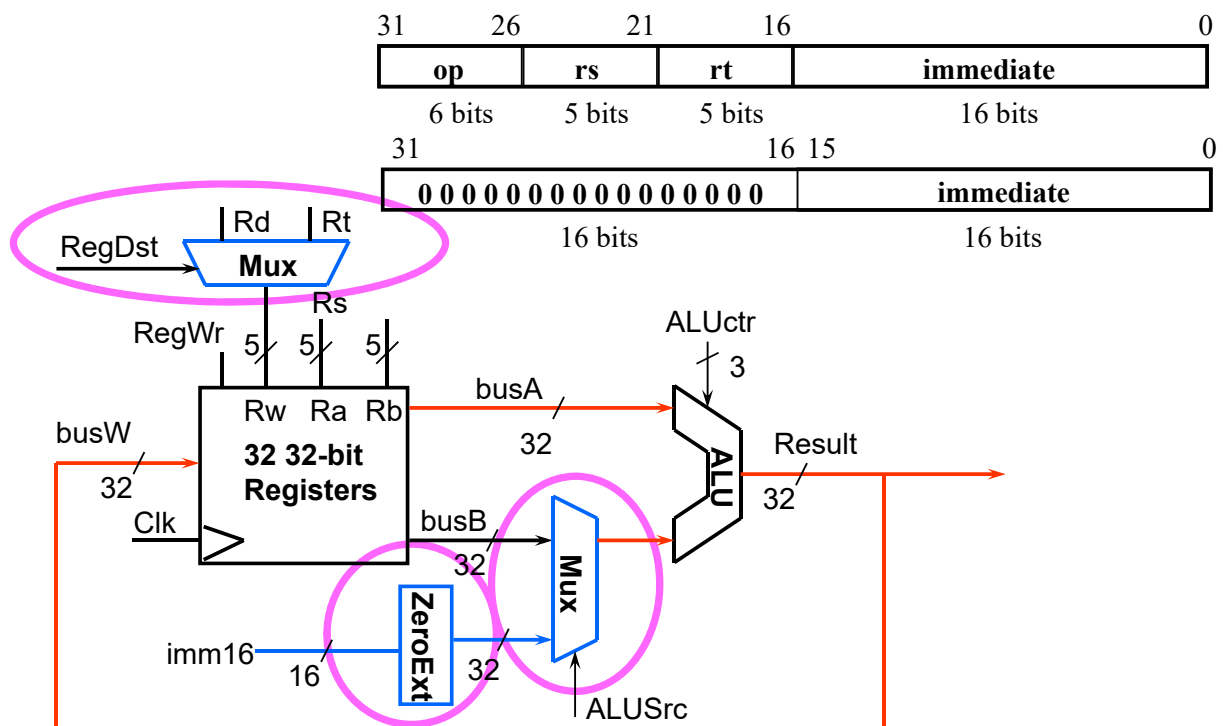- $R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$ Example : ori rt, rs, imm16




Datapath for Loads and Stores

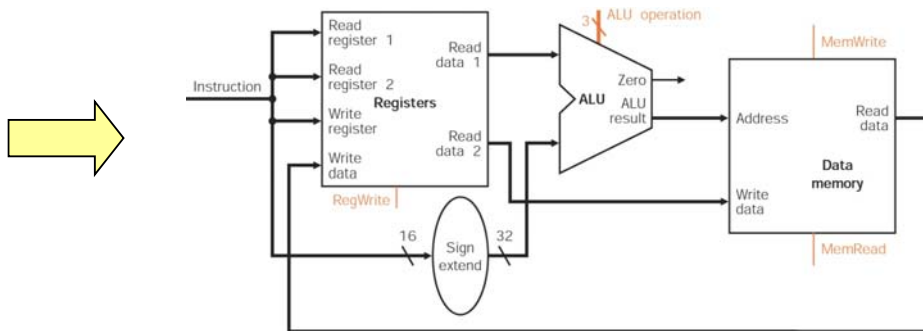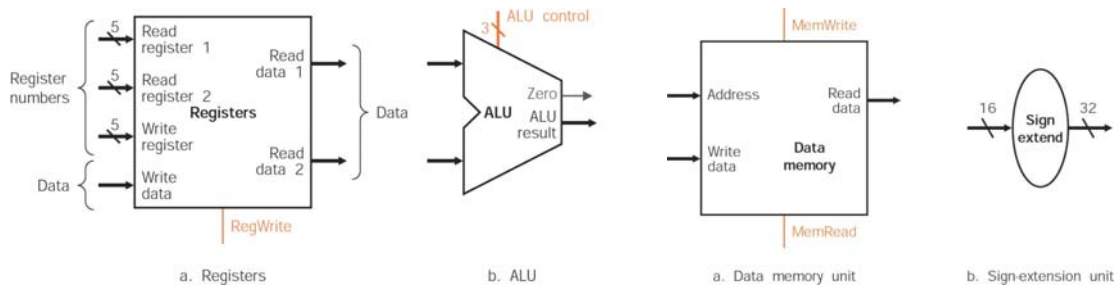

CE, KWU Prof. S.W. LEE 23

Load Operations

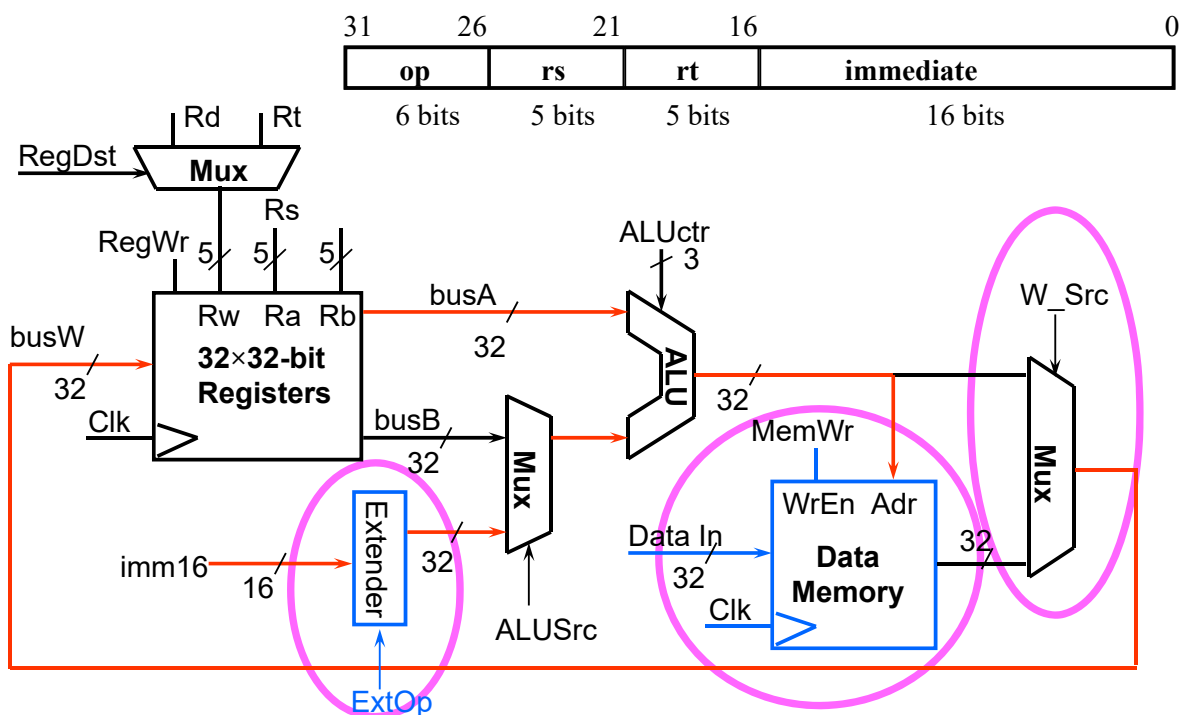
- $R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$ Example: `lw rt, rs, imm16`



CE, KWU Prof. S.W. LEE 24

Store Operations

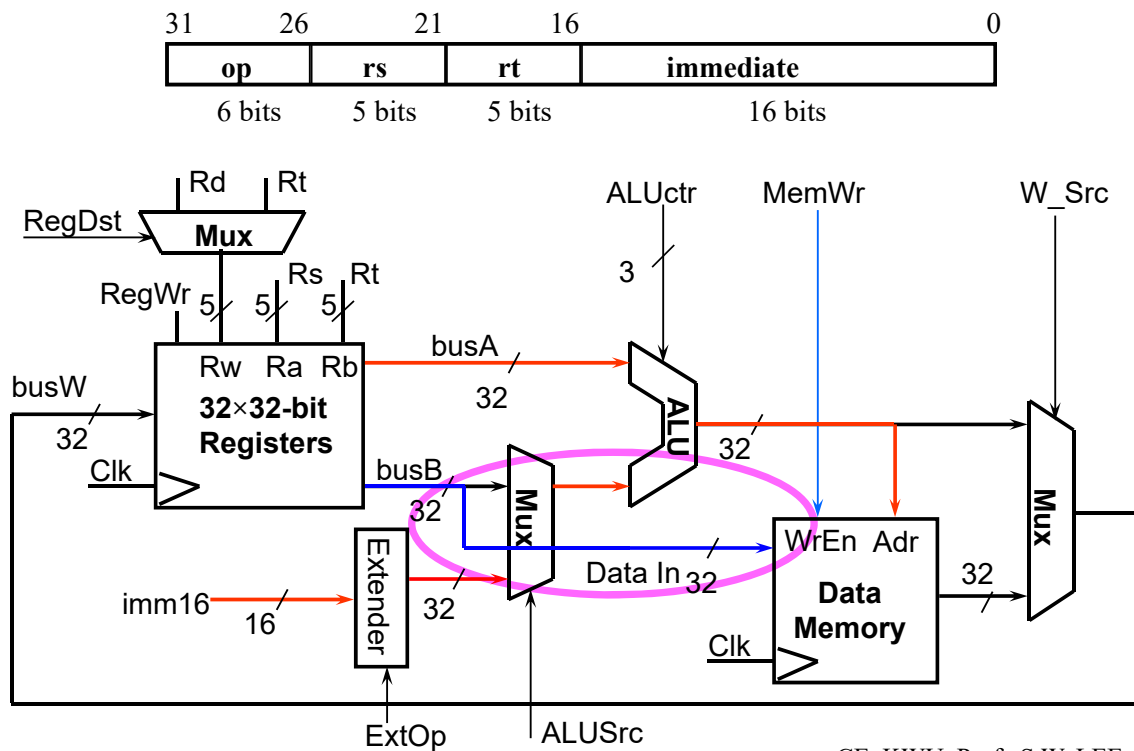- Mem[R[rs] + SignExt[imm16] ← R[rt]] Example: sw rt, rs, imm16



CE, KWU Prof. S.W. LEE 25

Datapath for Branch

- beq rs, rt, imm16

- mem[PC]
- Equal = R[rs] == R[rt]
- if (COND eq 0)

Fetch the instruction from memory



Calculate the branch condition

Calculate the next instruction's address


$$PC \leftarrow PC + 4 + (\text{SignExt}(\text{imm16}) \times 4)$$


else

$$PC \leftarrow PC + 4$$

 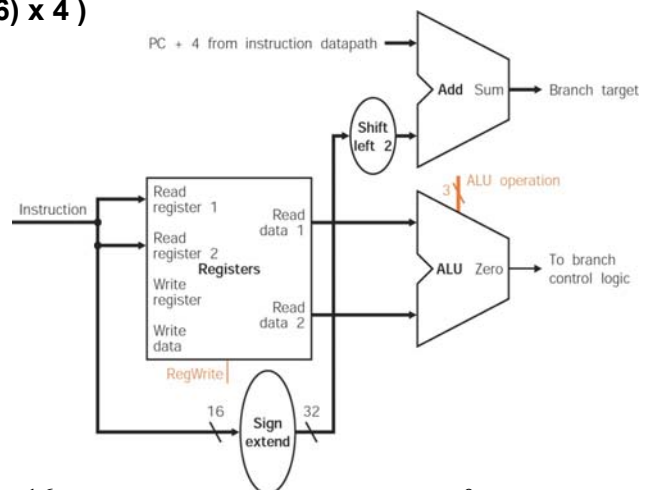

CE, KWU Prof. S.W. LEE 26

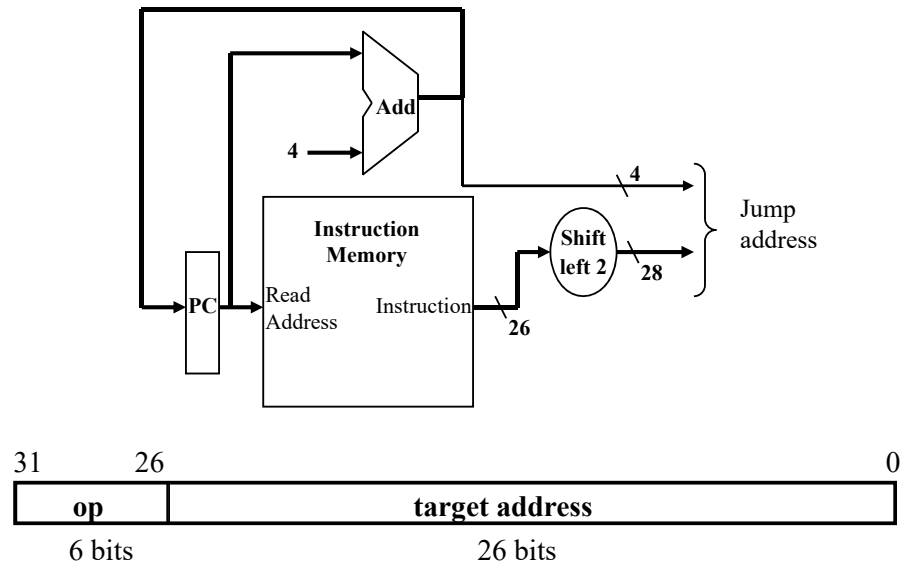

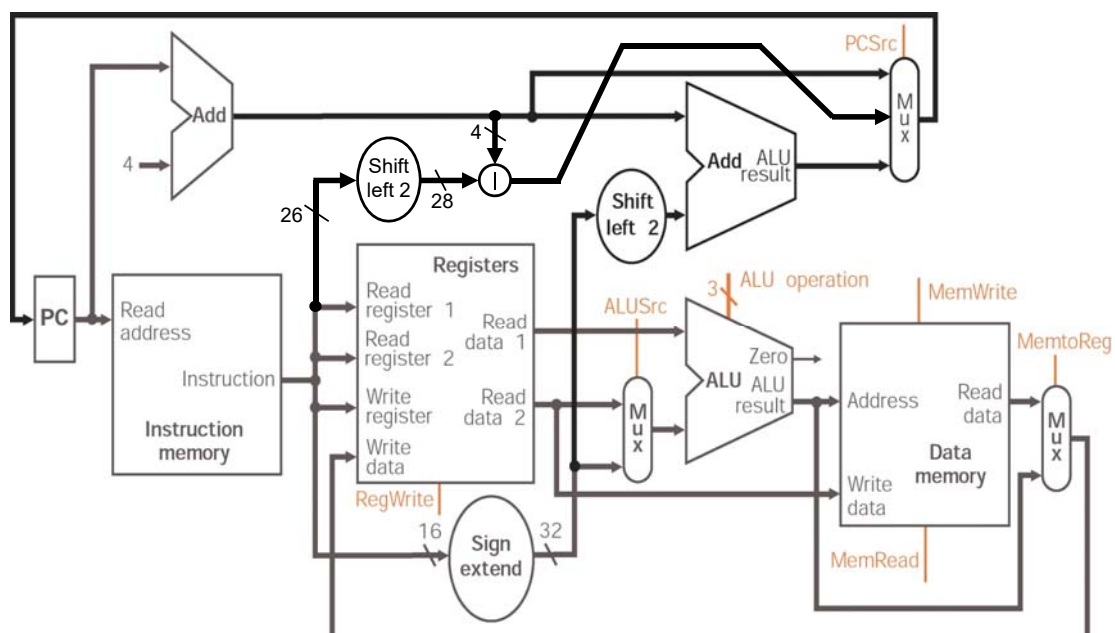

Creating a Single Datapath from the Parts

- **Assemble the datapath segments and add control lines and multiplexors as needed**
- **Single cycle design – fetch, decode and execute each instructions in one clock cycle**
 - **no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)**
 - **multiplexors needed at the input of shared elements with control lines to do the selection**
 - **write signals to control writing to the Register File and Data Memory**
- **Cycle time is determined by length of the longest path**