

---

## Chapter Four – I (3/4)

1

### Where we are headed


---

- **Single Cycle Problems:**
  - The clock cycle is equal to the worst-case delay for all instructions
  - Inefficient both in its performance and in its hardware cost
- **One Solution:**
  - use a “smaller” cycle time
  - have different instructions take different numbers of cycles
  - a “multicycle” datapath:

# What's wrong with our CPI=1 processor?

- Long Cycle Time
- All instructions take as much time as the slowest
- Real memory is not so nice as our idealized memory
  - cannot always get the job done in one (short) cycle

Arithmetic & Logical

 


Load



← Critical Path →

Store

 


Branch



CE, KWU Prof. S.W. LEE 3
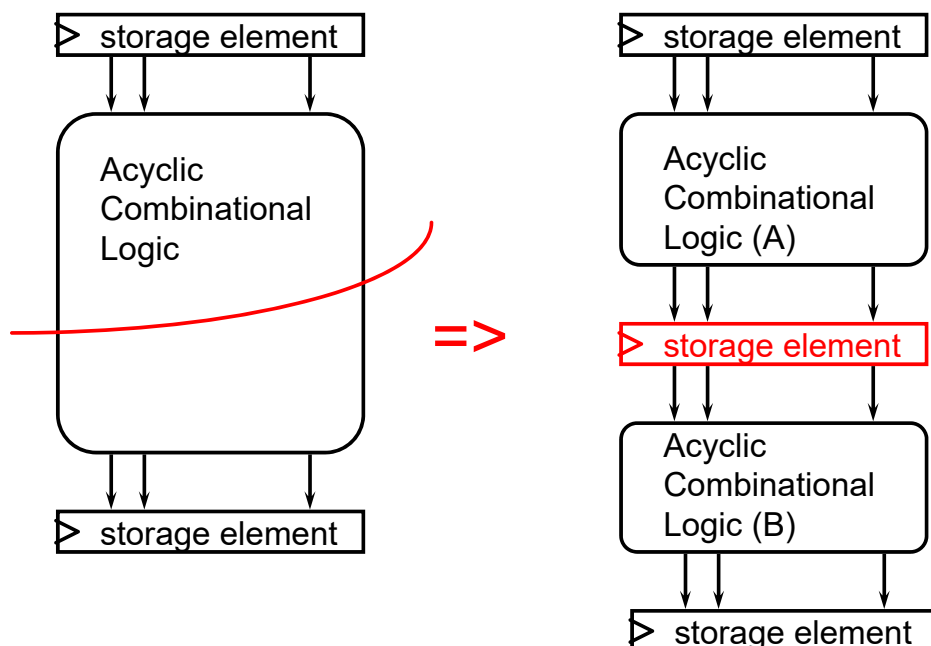
## Reducing Cycle Time

- Cut combinational dependency graph and insert register / latch
- Do same work in two fast cycles, rather than one slow one



CE, KWU Prof. S.W. LEE 4

# Multicycle Approach


---

- We will be reusing functional units
  - ALU used to compute address and to increment PC
  - Memory used for instruction and data
- Our control signals will not be determined directly by instruction
  - e.g., what should the ALU do for a “subtract” instruction?
- We’ll use a finite state machine for control
- Partition data so can handle different instruction execution times.
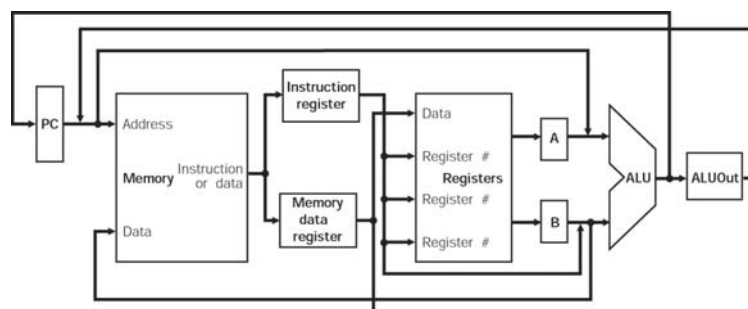
## Multicycle Implementation


---

- Break each instruction into a series of steps
  - Break it down into steps following our rule that data flows through at most one major functional unit (e.g., balance work across steps)
- Each step in the execution will take 1 clock cycle
  - Introduce new registers as needed (e.g, A, B, ALUOut, MDR, etc.)
- Allows a functional unit to be used more than once per instruction
  - Reduce the amount of hardware required
- Single memory unit
- Single ALU
- Registers after every major functional unit


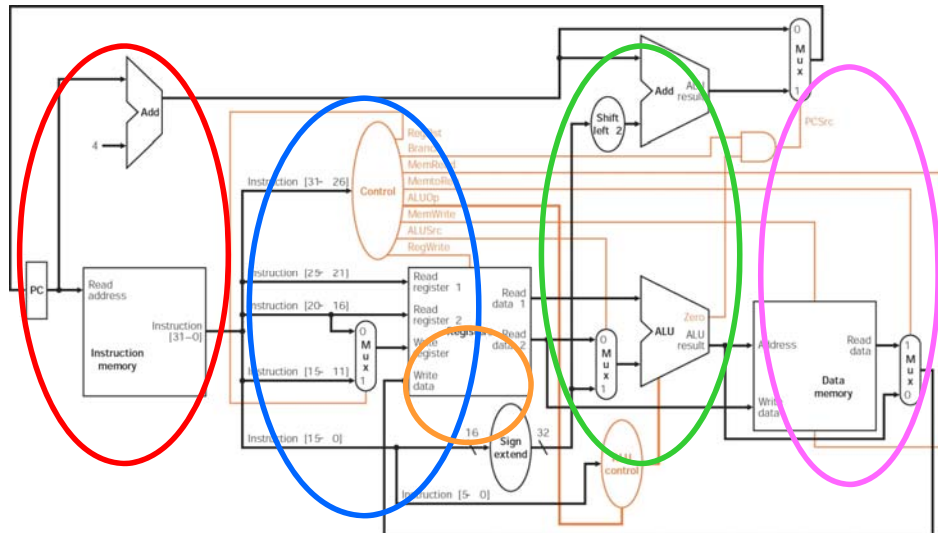
# Five Execution Steps

- Instruction Fetch (IF)
- Instruction Decode (ID) and Register Fetch
- Execution, Memory Address Computation, or Branch Completion (EX)
- Memory Access (MEM) or R-type instruction completion
- Write-back step (WB)




CE, KWU Prof. S.W. LEE

7

## Partitioning the CPI=1 Datapath

- Add registers between smallest steps

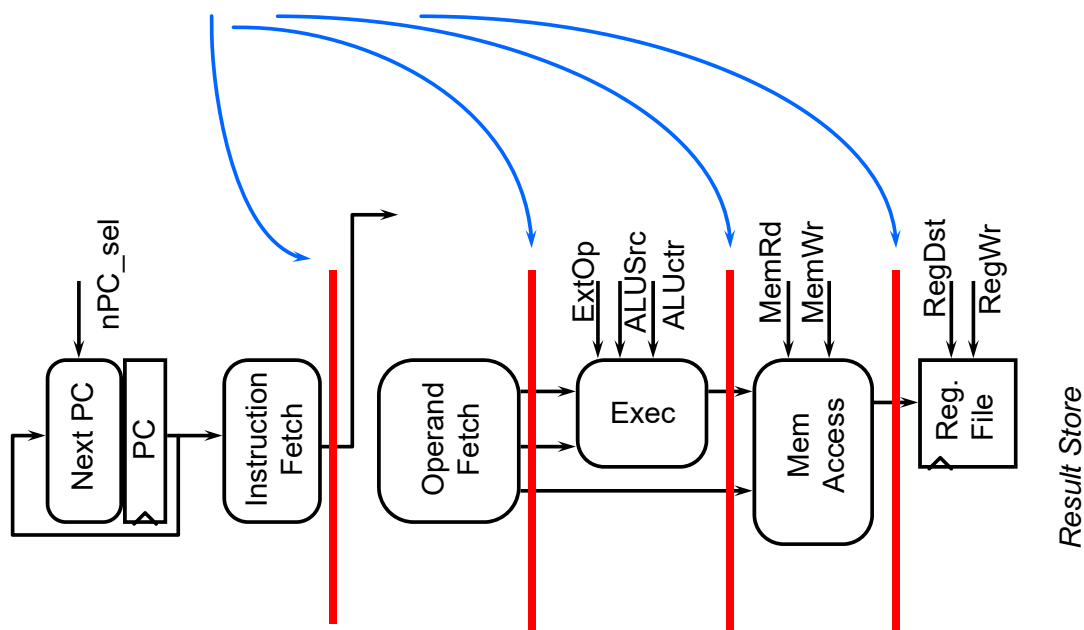

Allow the instruction to take multiple cycles.

CE, KWU Prof. S.W. LEE

8

## Step 1: Instruction Fetch

---

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR ← Memory[PC];  
PC ← PC + 4;
```

*Updating the PC at this stage can be done using ALU.*

## Step 2: Instruction Decode and Register Fetch

---

- Read registers `rs` and `rt` in case we need them
- Compute the branch address in case the instruction is a branch  
RTL:

```
A ← Reg[IR[25:21]];
B ← Reg[IR[20:16]];
ALUOut ← PC + (sign_extend(IR[15:0]) << 2);
```

- We aren't setting any control lines based on the instruction type  
(we are busy "decoding" it in our control logic)

## Step 3: (Instruction dependent operations)

---

- ALU is performing one of three functions, based on instruction type

- Memory Reference:

$ALUOut \leftarrow A + \text{sign-extend}(IR[15:0]);$

- R-type:

$ALUOut \leftarrow A \text{ op } B;$

- Branch:

$\text{if } (A==B) \text{ PC} \leftarrow ALUOut;$

- Jump instruction

$PC \leftarrow PC[31:28] \parallel (IR[25:0] \ll 2);$

## Step 4: (R-type or memory-access)

---

- Loads and stores access memory

$MDR \leftarrow \text{Memory}[ALUOut];$

or

$\text{Memory}[ALUOut] \leftarrow B;$

- R-type instructions finish

$\text{Reg}[IR[15:11]] \leftarrow ALUOut;$

*The write actually takes place at the end of the cycle on the edge*

## Step 5: Write-back step

---

- Load instructions finish

$\text{Reg}[\text{IR}[20:16]] \leftarrow \text{MDR};$


*What about all the other instructions?*

## Summary:

---


Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	$\text{IR} = \text{Memory}[\text{PC}]$ $\text{PC} = \text{PC} + 4$			
Instruction decode/register fetch	$A = \text{Reg}[\text{IR}[25:21]]$ $B = \text{Reg}[\text{IR}[20:16]]$ $\text{ALUOut} = \text{PC} + (\text{sign\_extend}(\text{IR}[15:0]) \ll 2)$			
Execution, address computation, branch/jump completion	$\text{ALUOut} = A \text{ op } B$	$\text{ALUOut} = A + \text{sign\_extend}(\text{IR}[15:0])$	if $(A == B)$ then $\text{PC} = \text{ALUOut}$	$\text{PC} = \text{PC}[31:28] \parallel (\text{IR}[25:0] \ll 2)$
Memory access or R-type completion	$\text{Reg}[\text{IR}[15:11]] = \text{ALUOut}$	Load: $\text{MDR} = \text{Memory}[\text{ALUOut}]$ or Store: $\text{Memory}[\text{ALUOut}] = B$		
Memory read completion		Load: $\text{Reg}[\text{IR}[20:16]] = \text{MDR}$		
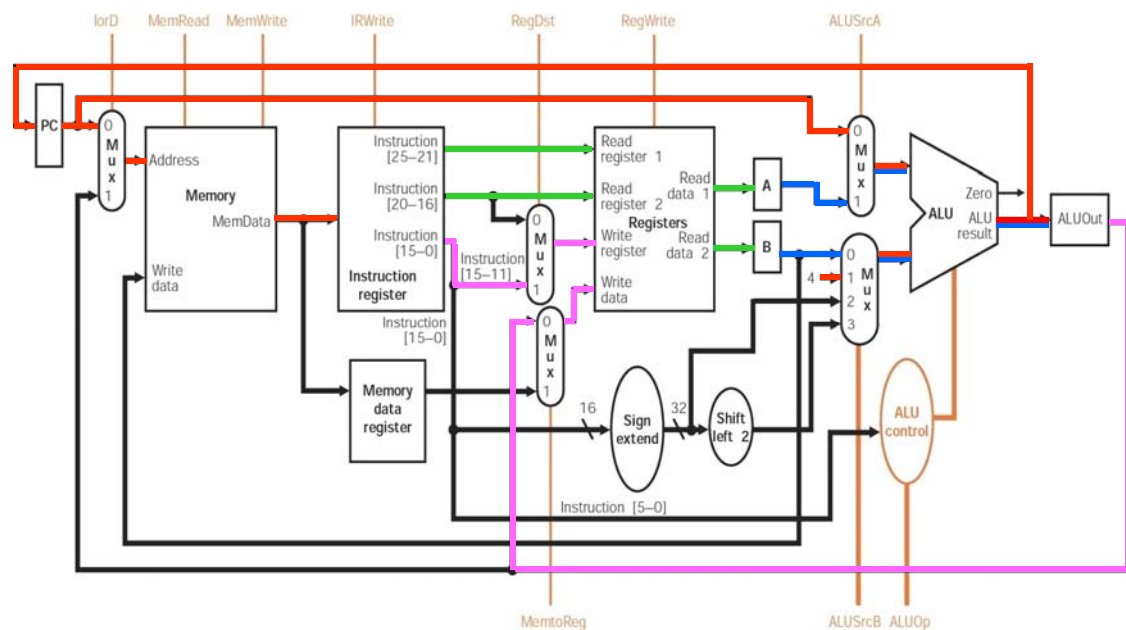
# Multicycle Datapath for R-type Instruction



CE, KWU Prof. S.W. LEE 15

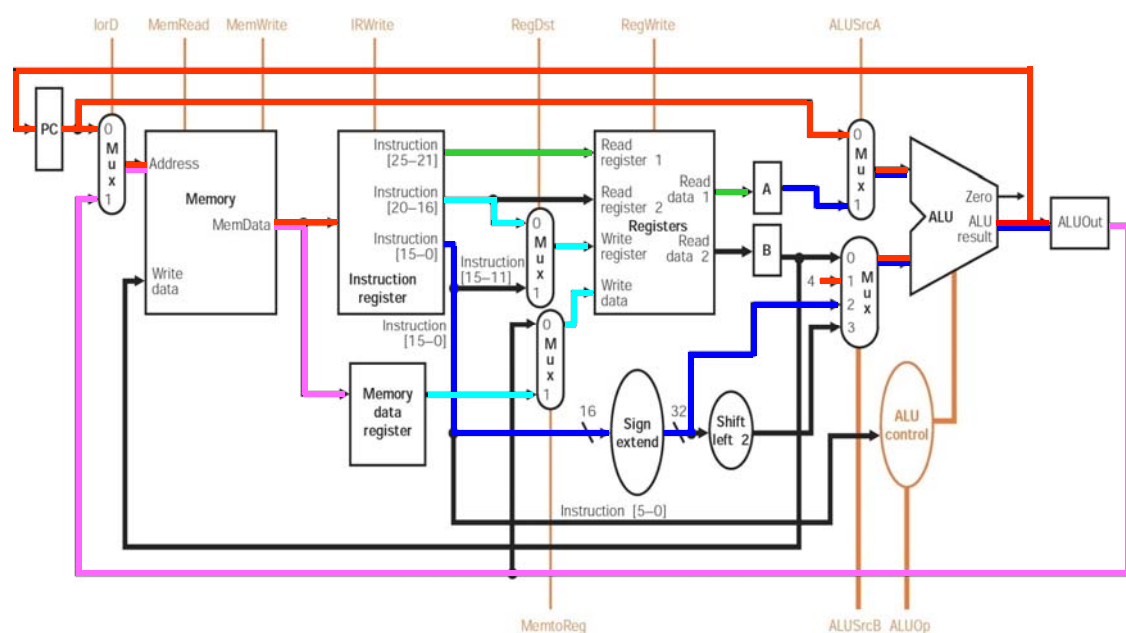
# Multicycle Datapath for Load Instruction



CE, KWU Prof. S.W. LEE 16



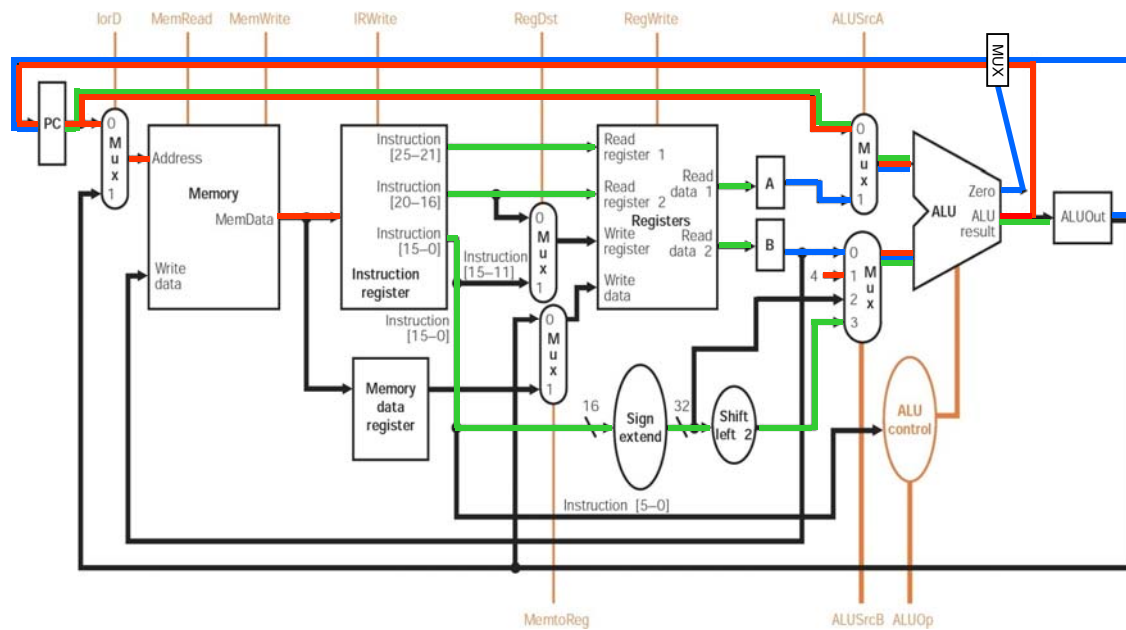
# Multicycle Datapath for Branch Instruction



CE, KWU Prof. S.W. LEE 17

# Multicycle Datapath with Control Lines

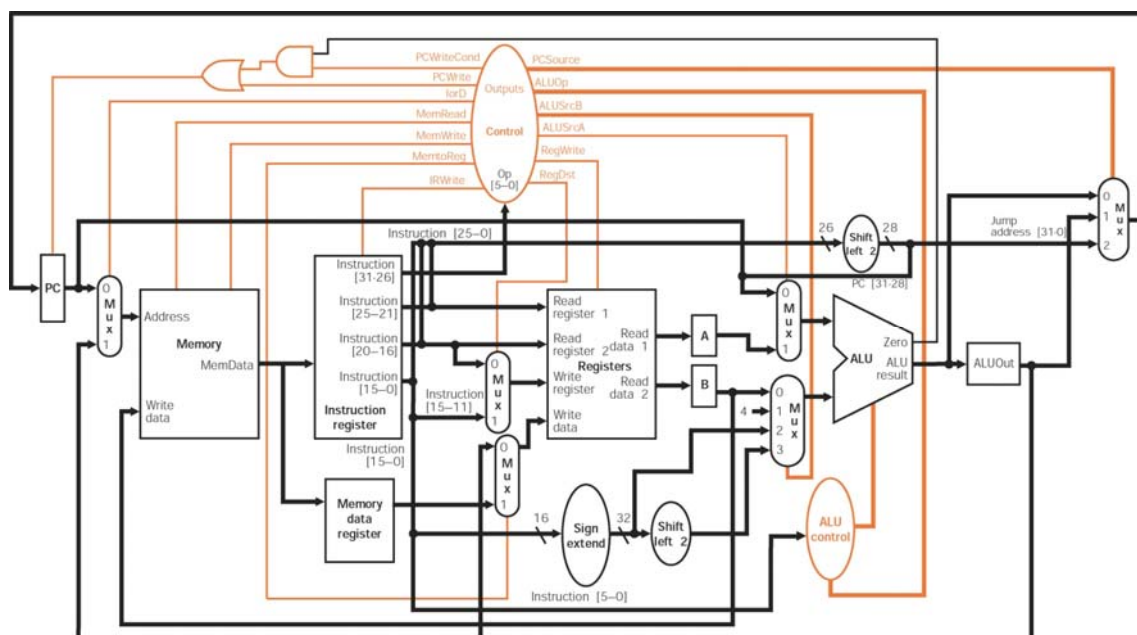


CE, KWU Prof. S.W. LEE 18

# Control for Multicycle Implementation


- Two techniques
  - Finite State Machine
  - Microprogramming

Mealy FSM:

 

- Finite state machines:
  - a set of states and
  - next state function (determined by current state and the input)
  - output function (determined by current state and possibly input)
  - a Moore machine (output based only on current state)
  - a Mealy machine (output based on current state & inputs)


Moore FSM:

 

CE, KWU Prof. S.W. LEE


19

# Control for Multicycle Implementation

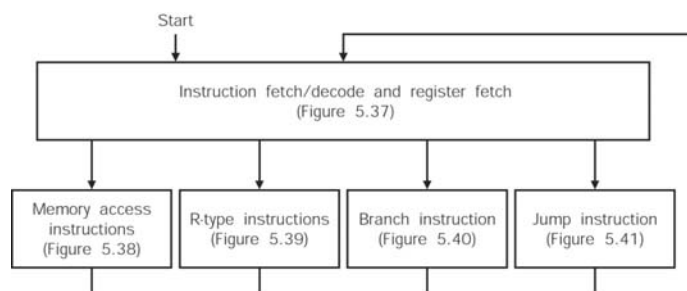



CE, KWU Prof. S.W. LEE

20

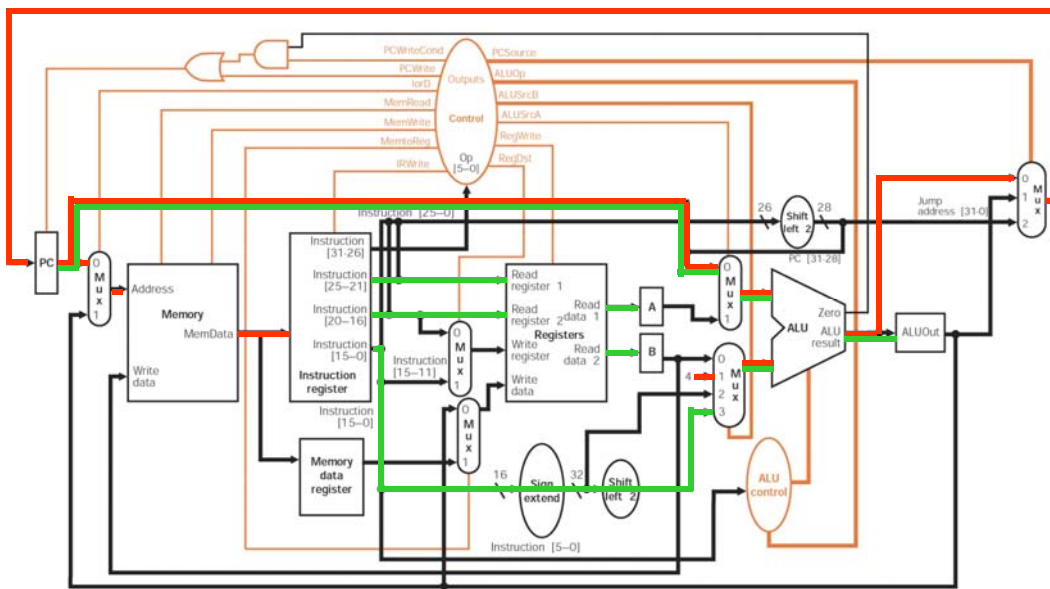


## Instruction Fetch and Decode


71 CE, KWU Prof. S.W. LEE

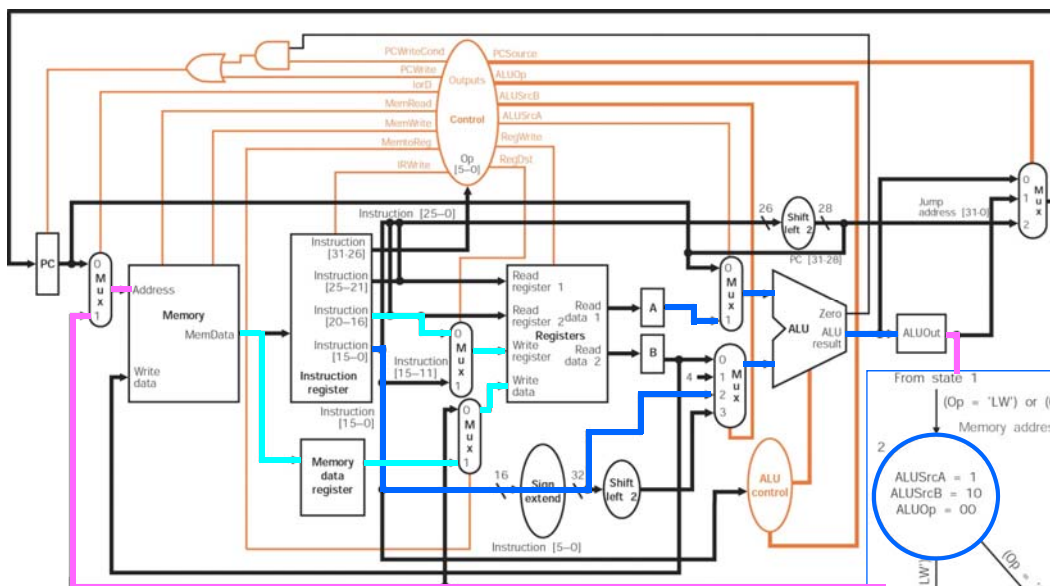 


## Memory Reference Instructions (load)


72 CE, KWU Prof. S.W. LEE

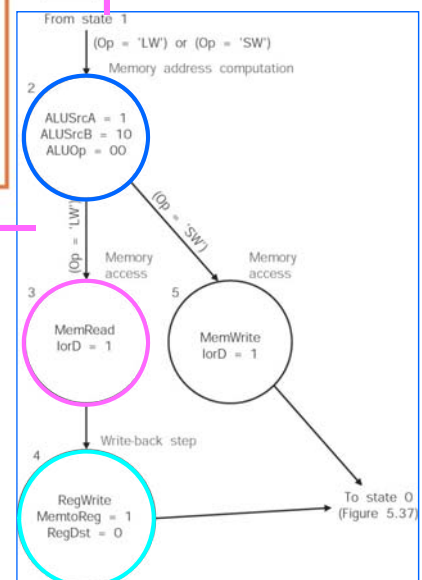

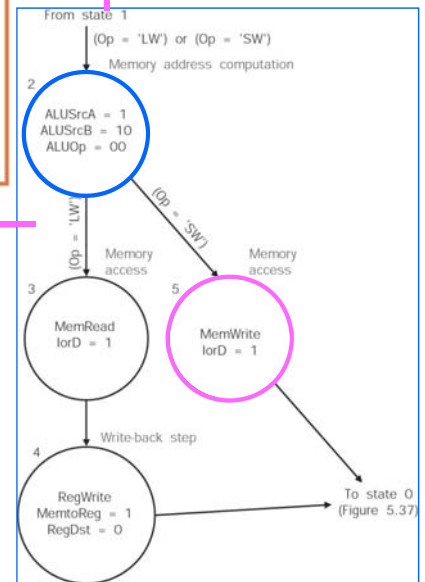


73 CE, KWU Prof. S.W. LEE

 


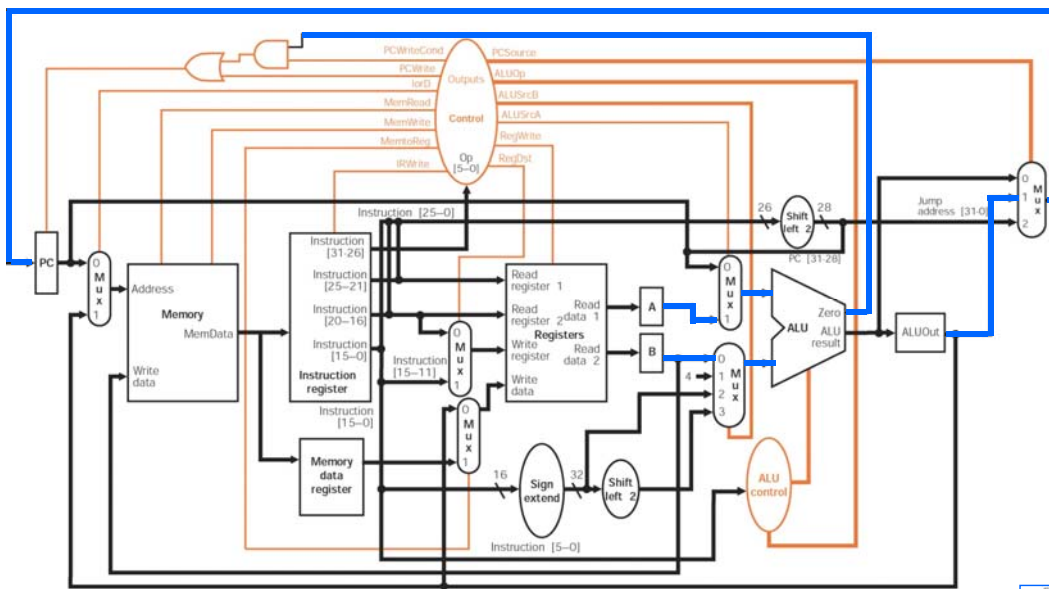


## Branch Instructions

 

CE, KWU Prof. S.W. LEE 25

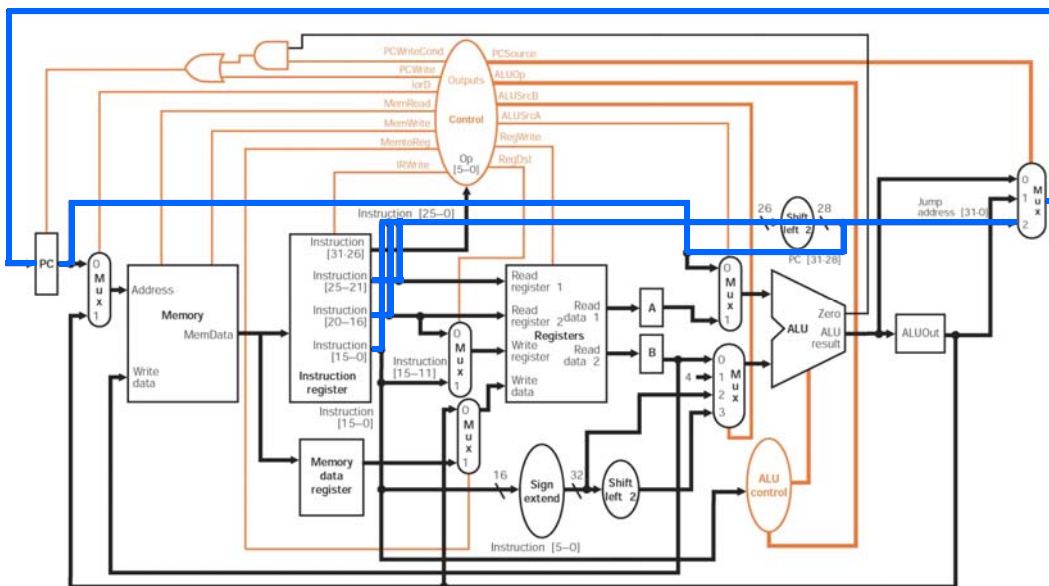

## Jump Instructions

 


CE, KWU Prof. S.W. LEE 26

# Implementing the Control


- Value of control signals is dependent upon:
  - what instruction is being executed
  - which step is being performed
- Use the information we've accumulated to specify a finite state machine
  - specify the finite state machine graphically, or
  - use microprogramming
- Implementation can be derived from specification

## Complete Finite State Machine Control

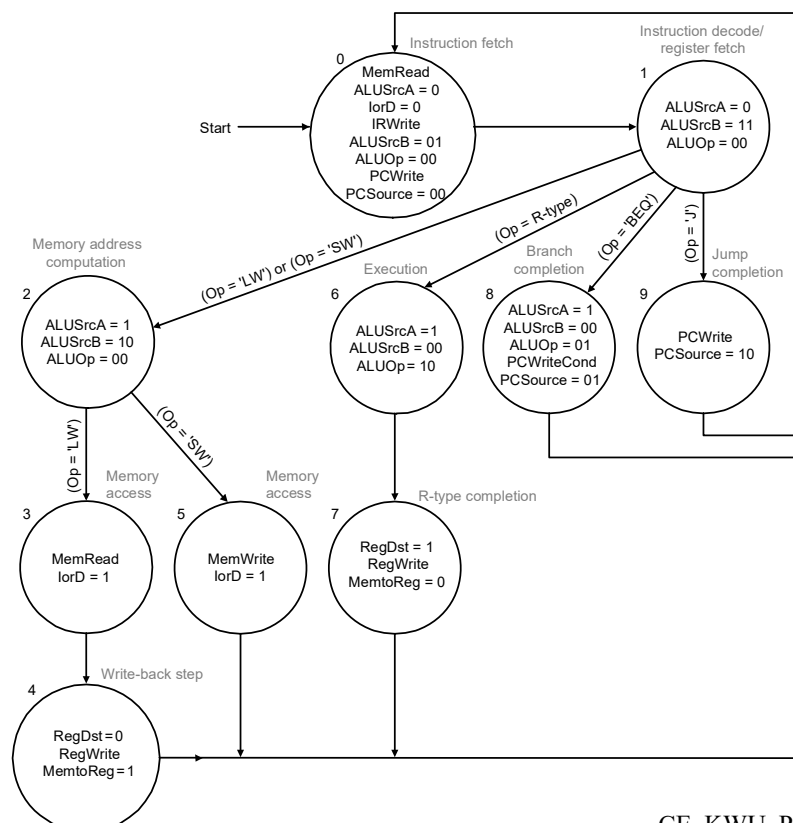


# Finite State Machine for Control

- Implementation:

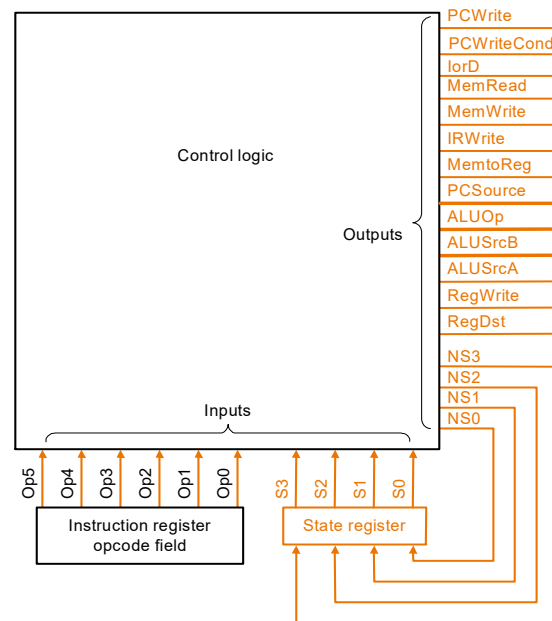

CE, KWU Prof. S.W. LEE 29
 
## Recap: PLA Implementation of the Main Control



CE, KWU Prof. S.W. LEE 30

# PLA Implementation

- If I picked a horizontal or vertical line could you explain it?

