 

Chapter Three (1/2)

1

Arithmetic for Computers

- Where we've been:
 - Abstractions:
 - Instruction Set Architecture
 - Assembly Language and Machine Language
- What's up ahead:
 - Implementing the Architecture



Numbers

- Bits are just bits (no inherent meaning)
 - conventions define relationship between bits and numbers
- Binary numbers (base 2)
0000 0001 0010 0011 0100 0101 0110 0111
MSB(most significant bit) LSB(least significant bit)
Of course it gets more complicated:
 - numbers are finite (overflow)
 - fractions and real numbers
 - negative numbers
 - e.g., no MIPS subi instruction; addi can add a negative number)
- How do we represent negative numbers?
 - i.e., which bit patterns will represent which numbers?

CE, KWU Prof. S.W. LEE 3

Binary-to-Hexadecimal Conversion

- ECA8 6420
- E – 1110
C – 1100
A – 1010
8 – 1000
6 – 0110
4 – 0100
2 – 0010
0 – 0000
- 1110 1100 1010 1000 0110 0100 0010 0000

Hex	Binary
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
A (10)	1010
B (11)	1011
C (12)	1100
D (13)	1101
E (14)	1110
F (15)	1111

Possible Representations

• Sign Magnitude	1's Complement	2's Complement
000 = +0	000 = +0	000 = +0
001 = +1	001 = +1	001 = +1
010 = +2	010 = +2	010 = +2
011 = +3	011 = +3	011 = +3
100 = -0	100 = -3	100 = -4
101 = -1	101 = -2	101 = -3
110 = -2	110 = -1	110 = -2
111 = -3	111 = -0	111 = -1

- Issues: balance, number of zeros, ease of operations
- Sign-magnitude
 - Where to put the sign bit? To the left? To the right?
 - Extra step to set the sign in arithmetic operations
 - Two zeros (positive zero, negative zero)???
- Which one is best?

Two's Complement Operations

- Negating a two's complement number: invert all bits and add 1
 - remember: “negate” and “invert” are quite different!
- $4 \rightarrow -4$
 $4 = 0000\ 0100$
 $-4 = 1111\ 1011 + 1$
 $= 1111\ 1100$
- $-4 \rightarrow 4$
 $-4 = 1111\ 1100$
 $4 = 0000\ 0011 + 1$
 $= 0000\ 0100$

MIPS

- 32 bit signed numbers:

```
0000 0000 0000 0000 0000 0000 0000 0000two = 0ten
0000 0000 0000 0000 0000 0000 0000 0001two = + 1ten
0000 0000 0000 0000 0000 0000 0000 0010two = + 2ten
...
0111 1111 1111 1111 1111 1111 1111 1110two = + 2,147,483,646ten
0111 1111 1111 1111 1111 1111 1111 1111two = + 2,147,483,647ten ← maxint
1000 0000 0000 0000 0000 0000 0000 0000two = - 2,147,483,648ten
1000 0000 0000 0000 0000 0000 0000 0001two = - 2,147,483,647ten ← minint
1000 0000 0000 0000 0000 0000 0000 0010two = - 2,147,483,646ten
...
1111 1111 1111 1111 1111 1111 1111 1101two = - 3ten
1111 1111 1111 1111 1111 1111 1111 1110two = - 2ten
1111 1111 1111 1111 1111 1111 1111 1111two = - 1ten
```

- The value of a 32-bit number represented in 2's complement is:

$$(x_{31} * -2^{31}) + (x_{30} * 2^{30}) + (x_{29} * 2^{29}) + \dots + (x_1 * 2^1) + (x_0 * 2^0)$$

- The value of a 8-bit number (1111 1000) in 2's complement?

CE, KWU Prof. S.W. LEE 7

Signed Comparison

- \$s0 = 1111 1111 1111 1111 1111 1111 1111 1111
\$s1 = 0000 0000 0000 0000 0000 0000 0000 0001
- slt \$t0, \$s0, \$s1 # signed comparison
sltu \$t1, \$s0, \$s1 # unsigned comparison
- \$t0 = ?
\$t1 = ?
- \$s0 = 4294967295 or -1

CE, KWU Prof. S.W. LEE 8

Sign Extension

- Converting n bit numbers into numbers with more than n bits:
 - MIPS 16 bit immediate gets converted to 32 bits for arithmetic
 - copy the most significant bit (the sign bit) into the other bits

0010 -> 0000 0010
 1010 -> 1111 1010


- "sign extension" (lbu vs. lb)

lb \$t0, 0(\$s0)

\$t0 1111 ... 1 1000 0001

lbu \$t0, 0(\$s0)

\$t0 0000 ... 0 1000 0001

 

Addition & Subtraction

- Two's complement operations easy
 - subtraction using addition of negative numbers (9-6)

$$x - y = x + (-y)$$

$$\begin{array}{r} 0111 \qquad 0111 \\ - 0110 \qquad + 1010 \\ \hline \end{array}$$

- 6 = 0110 → -6 = 1010

- Overflow (result too large for finite computer word):
 - e.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 0111 \\ + 0001 \\ \hline 1000 \end{array} \quad \begin{array}{l} \text{note that overflow term is somewhat misleading,} \\ \text{it does not mean a carry "overflowed"} \end{array}$$

Overflow

- When adding or subtracting numbers, the sum or difference can go beyond the range of representable numbers.
- This is known as overflow. For example, for two's complement numbers,

5 = 0101	-5 = 1011	5 = 0101	-5 = 1011
+ 6 = 0110	+ -6 = 1010	- -6 = 1010	- +6 = 0110
-----	-----	-----	-----
-5 = 1011	5 = 0101	-5 = 1011	5 = 0101

- Overflow creates an incorrect result that should be detected.

Overflow Conditions

- No overflow when adding a positive and a negative number
- No overflow when signs are the same for subtraction
- Overflow occurs when the value affects the sign:

	A	B	Overflow if
A + B	≥ 0	≥ 0	Result < 0
A + B	< 0	< 0	Result ≥ 0
A - B	≥ 0	< 0	Result < 0
A - B	< 0	≥ 0	Result ≥ 0

- Consider the operations A + B, and A - B
 - Can overflow occur if B is 0 ?
 - Can overflow occur if A is 0 ?

2's Comp - Detecting Overflow

- When adding two's complement numbers, overflow will only occur if
 - the numbers being added have the same sign
 - the sign of the result is different

- If we perform the addition

$$\begin{array}{r} a_{n-1} \ a_{n-2} \ \dots \ a_1 \ a_0 \\ + \ b_{n-1} \ b_{n-2} \ \dots \ b_1 \ b_0 \\ \hline = \ s_{n-1} \ s_{n-2} \ \dots \ s_1 \ s_0 \end{array}$$

- Overflow can be detected as

$$V = a_{n-1} \cdot b_{n-1} \cdot \overline{s_{n-1}} + \overline{a_{n-1}} \cdot \overline{b_{n-1}} \cdot s_{n-1}$$

- Overflow can also be detected as

$$V = c_n \otimes c_{n-1}$$

where c_{n-1} and c_n are the carry in and carry out of the most significant bit.

Unsigned - Detecting Overflow

- For unsigned numbers, overflow occurs if there is carry out of the most significant bit.

$$V = c_n$$

- For example,

$$\begin{array}{r} 1001 = 9 \\ +1000 = 8 \\ \hline =0001 = 1 \end{array}$$


- With the MIPS architecture
 - Overflow exceptions occur for two's complement arithmetic
 - add, sub, addi
 - Overflow exceptions do not occur for unsigned arithmetic
 - addu, subu, addiu

Dealing with Overflow

- Some languages (e.g., C) ignore overflow
 - Use MIPS addu, addui, subu instructions
- Other languages (e.g., Ada, Fortran) require raising an exception
 - Use MIPS add, addi, sub instructions
 - On overflow, invoke exception handler
 - Save PC in exception program counter (EPC) register
 - Jump to predefined handler address
 - mfc0 (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action


An ALU (arithmetic logic unit)

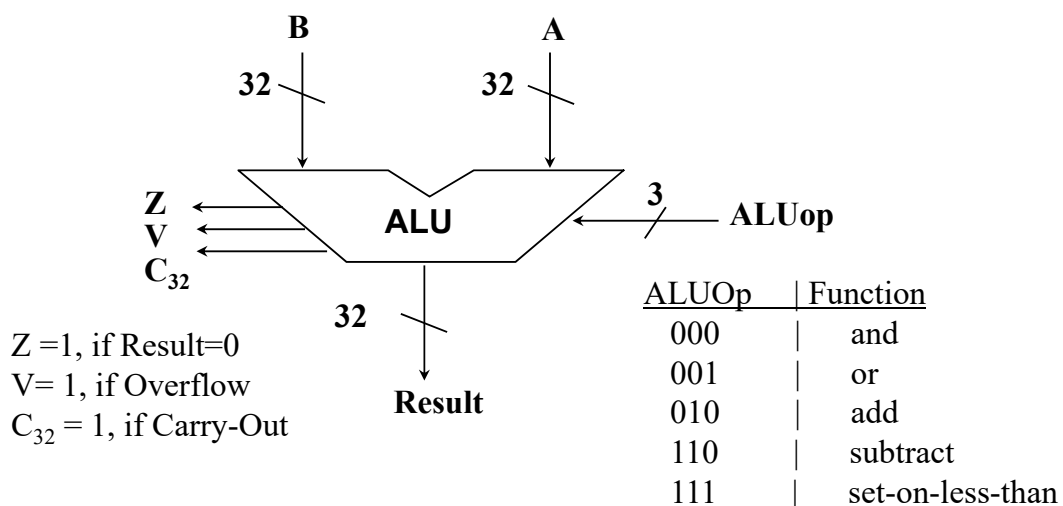- Let's build an ALU to support the and, or, add, sub, beq instructions
 - we'll just build a 1 bit ALU, and use 32 of them



1-Bit and 32-Bit ALU

For AND, OR,
& Addition

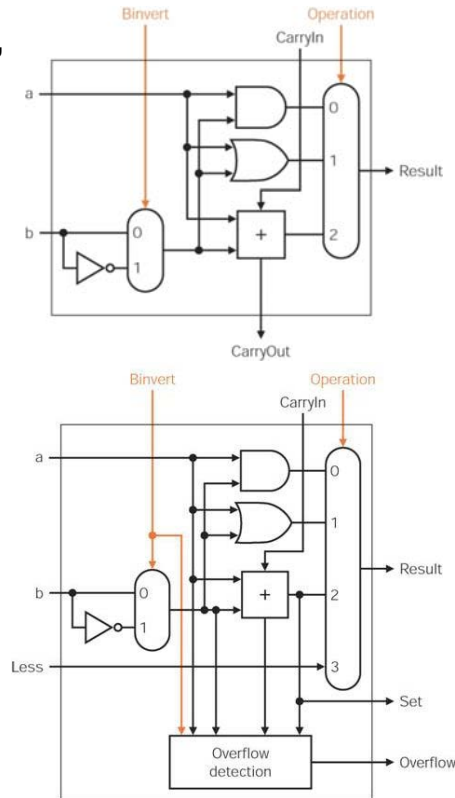

$$set = (A < B)$$



$$V = c_n \otimes c_{n-1}$$

CE, KWU Prof. S.W. LEE

17

Adding a NOR & SLT

 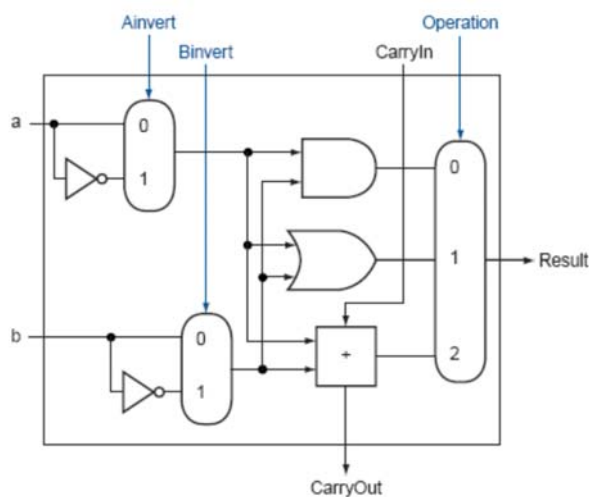
- Choose to invert a to get “a NOR b”
- Need to support the set-on-less-than instruction (slt)



CE, KWU Prof. S.W. LEE

18

Supporting SLT

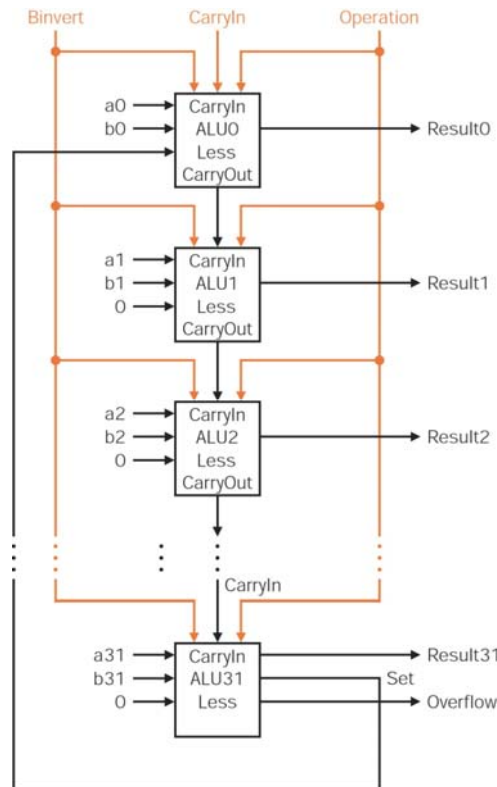


CE, KWU Prof. S.W. LEE 19

Test for equality

- Need to support test for equality (beq \$t5, \$t6, \$t7)
 - Use comparison:
 - xor all corresponding bits
 - Or use subtraction:
 - $(a-b) = 0$ implies $a = b$
- Checking if zero costs a lot.
- Notice control lines:

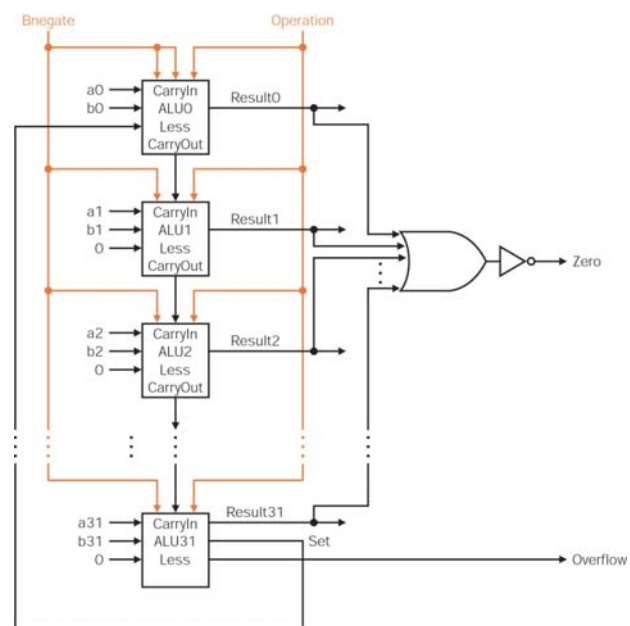000 = and
 001 = or
 010 = add
 110 = subtract
 111 = slt



•Note: zero is a 1 when the result is zero!

CE, KWU Prof. S.W. LEE 20

ALU Summary

- We can build an ALU to support MIPS addition
- Our focus is on comprehension, not performance
- Real processors use more sophisticated techniques for arithmetic
- Where performance is not critical, hardware description languages allow designers to completely automate the creation of hardware!

```
module MIPSALU (ALUctl, A, B, ALUOut, Zero);
    input [3:0] ALUctl;
    input [31:0] A,B;
    output reg [31:0] ALUOut;
    output Zero;
    assign Zero = (ALUOut==0); //Zero is true if ALUOut is 0; goes anywhere
    always @(ALUctl, A, B) //reevaluate if these change
        case (ALUctl)
            0: ALUOut <= A & B;
            1: ALUOut <= A | B;
            2: ALUOut <= A + B;
            6: ALUOut <= A - B;
            7: ALUOut <= A < B ? 1:0;
            12: ALUOut <= ~(A | B); // result is nor
            default: ALUOut <= 0; //default to 0, should not happen;
        endcase
endmodule
```


 


FIGURE B.4.3 A Verilog behavioral definition of a MIPS ALU. This could be synthesized using a module library containing basic arithmetic and logical operations.

 Problem: ripple carry adder is slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition?
 - two extremes: ripple carry & sum-of-products



Can you see the ripple? How could you get rid of it?

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0$$

$$c_2 = b_1 c_1 + a_1 c_1 + a_1 b_1$$

$$c_3 = b_2 c_2 + a_2 c_2 + a_2 b_2$$

$$c_4 = b_3 c_3 + a_3 c_3 + a_3 b_3$$

$$c_2 = b_1 (b_0 c_0 + a_0 c_0 + a_0 b_0) + a_1 (b_0 c_0 + a_0 c_0 + a_0 b_0) + a_1 b_1$$

$$c_3 = ???$$

$$c_4 = ?????$$

Not feasible! Why?

Carry Logic Equation

- The carry logic equation is

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

- We define a **propagate** signal

$$p_i = a_i + b_i$$

and a **generate** signal

$$g_i = a_i b_i$$

- This allows the carry logic equation to be rewritten as

$$c_{i+1} = g_i + p_i c_i$$

Carry-lookahead adder*

- An approach in-between our two extremes
- Goal:** To produce sum and carryout for n-th bit without waiting for a carry over from (n-1)th bit.
- How???
- For each bit position, we look into
 - whether a carry will be generated by itself? ($g_i = a_i b_i$)
 - whether a carryin could be propagated to the next bit position? ($p_i = a_i + b_i$)
- At each bit, CarryOut is now computed based on g_i and p_i , not on c_i

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1$$

$$c_3 = g_2 + p_2 c_2$$

$$c_4 = g_3 + p_3 c_3$$

$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$

Feasible! Why?

Various Adders

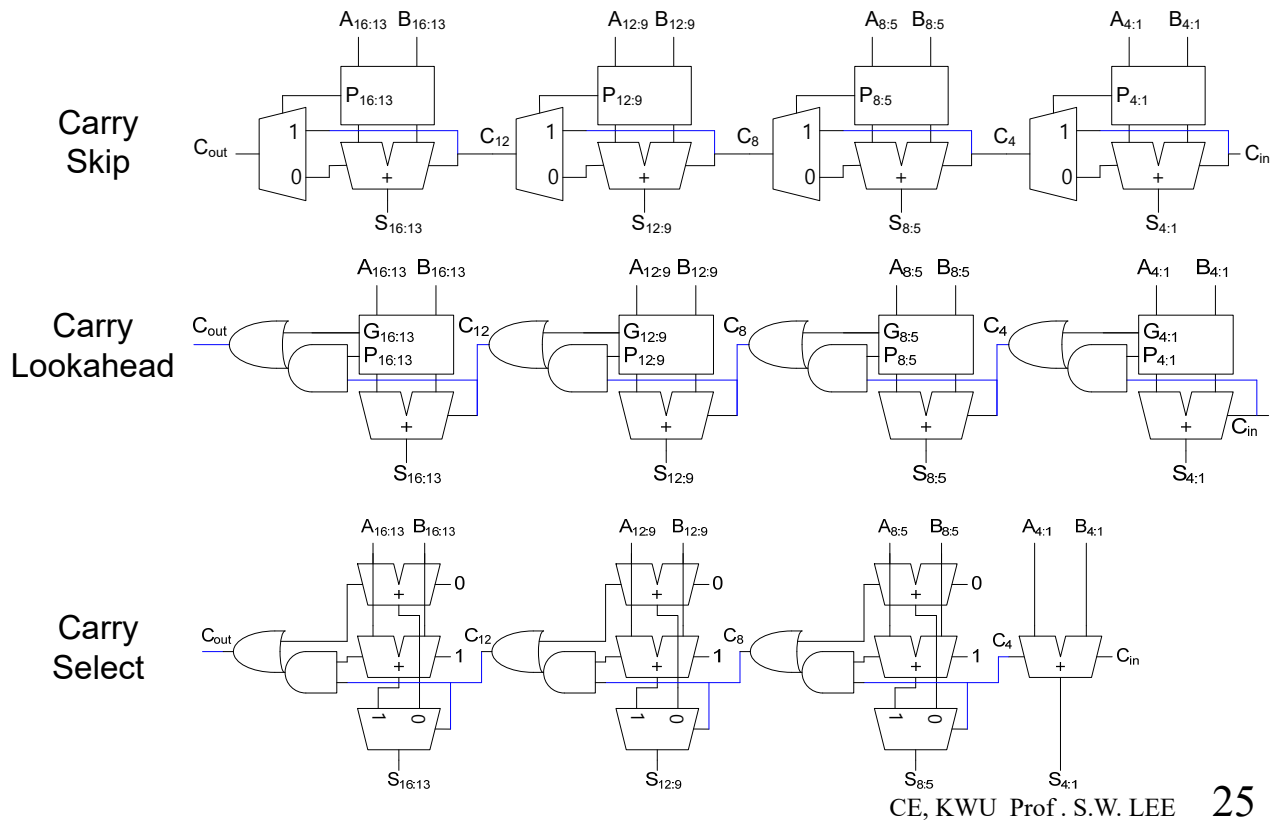


Arithmetic for Multimedia

- Graphics and media processing operates on vectors of 8-bit and 16-bit data
 - Use 64-bit adder, with partitioned carry chain
 - Operate on 8×8 -bit, 4×16 -bit, or 2×32 -bit vectors
 - SIMD (single-instruction, multiple-data)
- Saturating operations
 - On overflow, result is largest representable value
 - c.f. 2s-complement modulo arithmetic
 - E.g., clipping in audio, saturation in video

SIMD

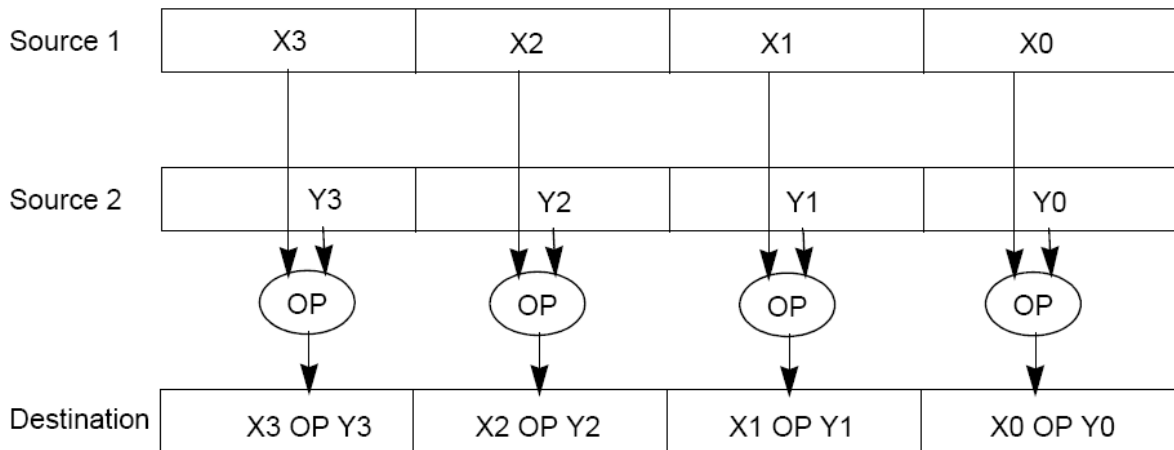- **SIMD (single instruction multiple data) architecture performs the same operation on multiple data elements in parallel**
- **PADDW MM0, MM1**



CE, KWU Prof. S.W. LEE 27

Conclusion

- **We can build an ALU to support the MIPS instruction set**
 - key idea: use multiplexor to select the output we want
 - we can efficiently perform subtraction using two's complement
 - An n -bit ALU can be designed by concatenating n 1-bit ALUs
- **Important points about hardware**
 - all of the gates are always working
 - the speed of a gate is affected by the number of inputs to the gate
 - the speed of a circuit is affected by the number of gates in series (on the “critical path” or the “deepest level of logic”)
 - Carry lookahead logic can be used to improve the speed of the computation.
 - A variety of design options exist for implementing the ALU.
- **The best design depends on area, delay, and power requirements, which vary based on the underlying technology.**

CE, KWU Prof. S.W. LEE 28