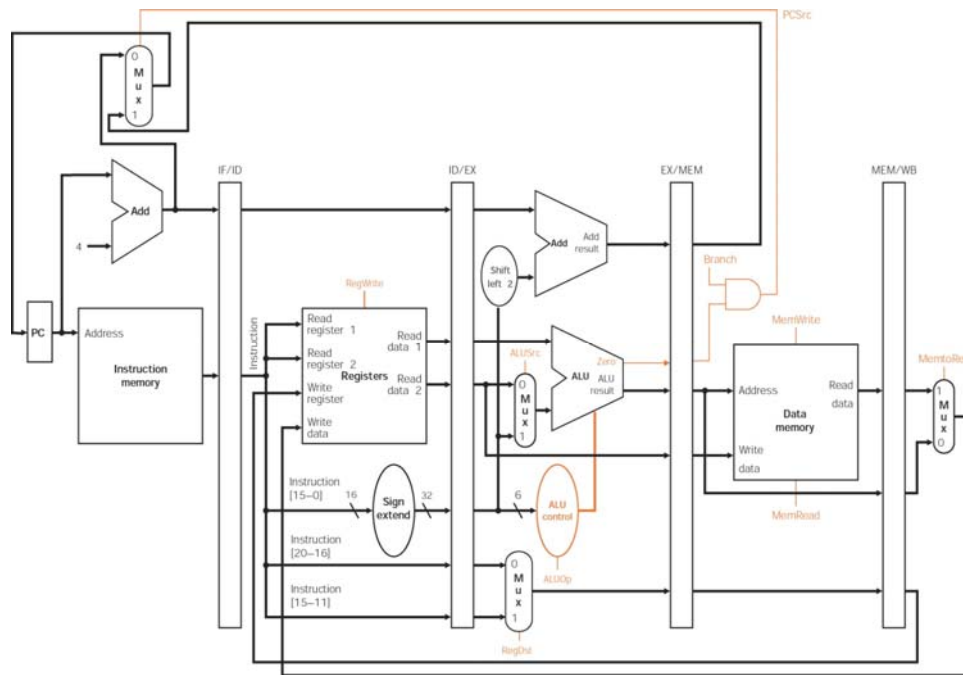

Chapter Four – II (3/5)

1

Pipeline control

- We have 5 stages. What needs to be controlled in each stage?
 - Instruction Fetch and PC Increment
 - Instruction Decode / Register Fetch
 - Execution
 - Memory Stage
 - Write Back
- How would control be handled in an automobile plant?
 - a fancy control center telling everyone what to do?
 - should we use a finite state machine?

Datapath with Control Signals



CE, KWU Prof. S.W. LEE 3

Pipeline Control: ALU Control Signals

| ALU control input | Function |
|-------------------|----------|
| 000 | AND |
| 001 | OR |
| 010 | Add |
| 110 | Sub |
| 111 | Slt |


| Op | ALUOp | Operation | Funct | ALU action | ALU control input |
|--------|-------|--------------|--------|------------|-------------------|
| LW | 00 | Load word | XXXXXX | add | 010 |
| SW | 00 | Store word | XXXXXX | add | 010 |
| BEQ | 01 | Branch equal | XXXXXX | sub | 110 |
| R-type | 10 | add | 100000 | add | 010 |
| R-type | 10 | sub | 100010 | sub | 110 |
| R-type | 10 | AND | 100100 | AND | 000 |
| R-type | 10 | OR | 100101 | OR | 001 |
| R-type | 10 | slt | 101010 | slt | 111 |

CE, KWU Prof. S.W. LEE 4

Pipeline Control


- Pass control signals along just like the data

| Instruction | Execution/Address Calculation stage control lines | | | | Memory access stage control lines | | | Write-back stage control lines | |
|-------------|---|------------|------------|------------|--------------------------------------|-------------|--------------|--------------------------------------|---------------|
| | Reg Dst | ALU Op1 | ALU Op0 | ALU Src | Branc h | Mem Read | Mem Write | Reg write | Mem to Reg |
| R-format | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| lw | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| sw | X | 0 | 0 | 1 | 0 | 0 | 1 | 0 | X |
| beq | X | 0 | 1 | 0 | 1 | 0 | 0 | 0 | X |

 


CE, KWU Prof. S.W. LEE 5

Datapath with pipelined control signals

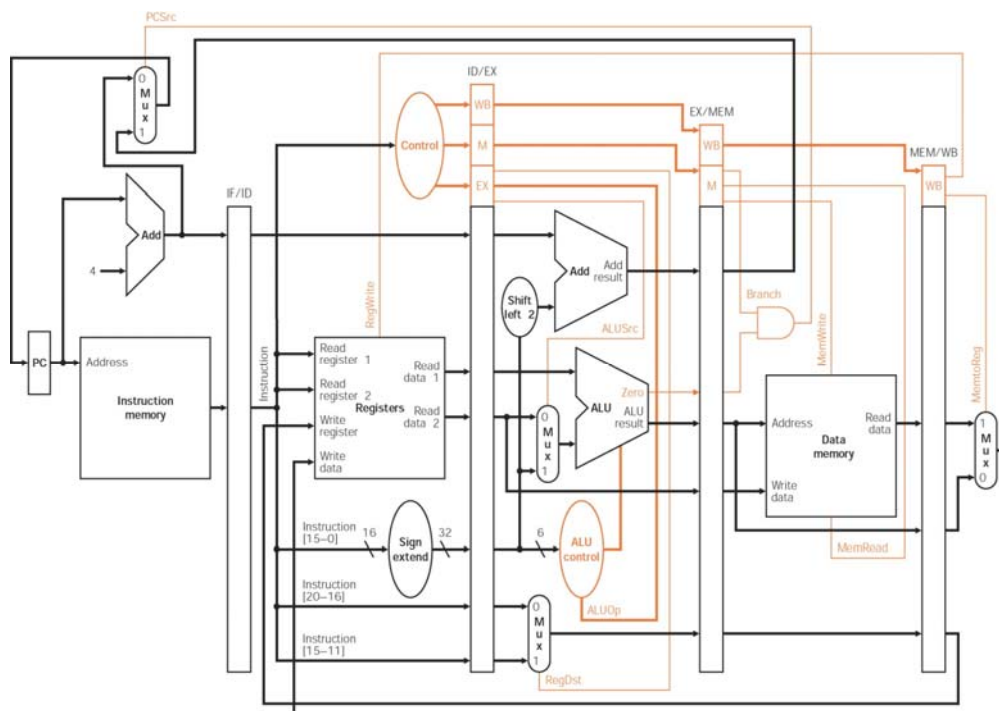


CE, KWU Prof. S.W. LEE 6

Execution Example (Clock 1)

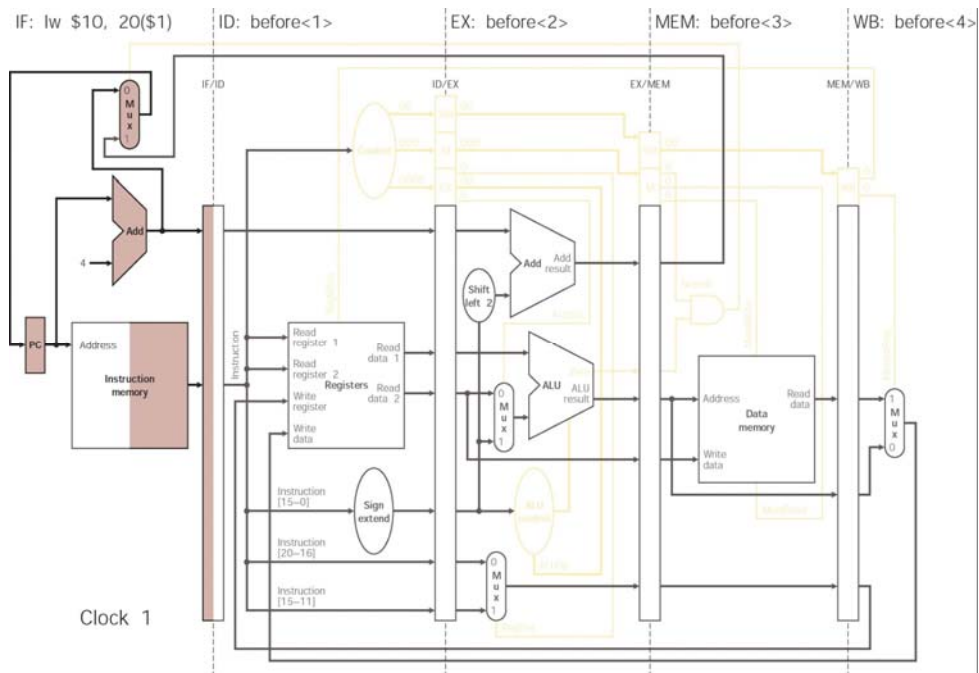


CE, KWU Prof. S.W. LEE 7

Execution Example (Clock 2)

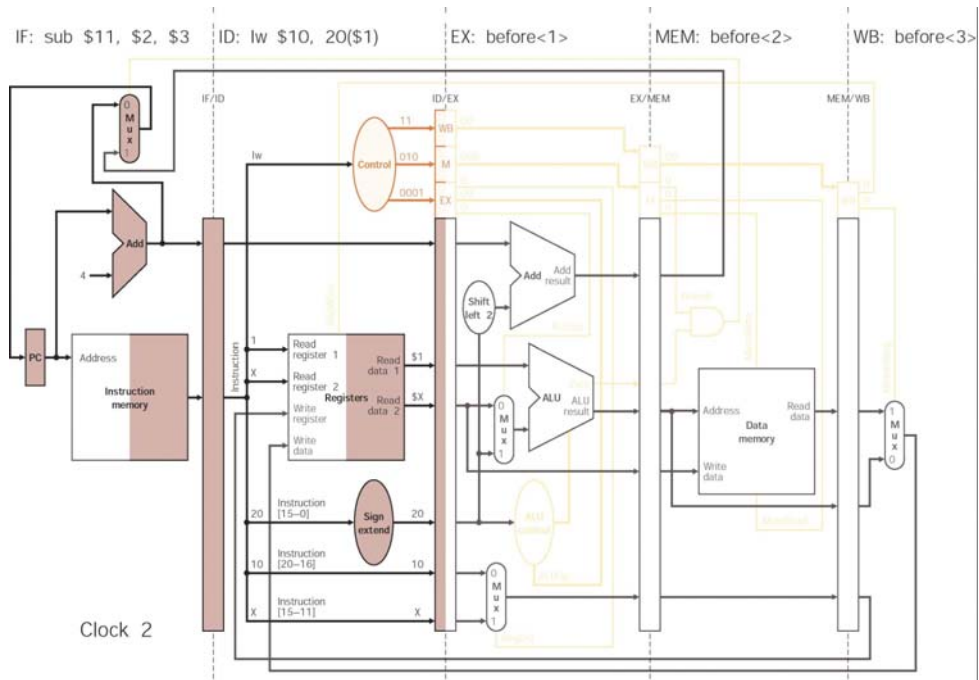


CE, KWU Prof. S.W. LEE 8

Execution Example (Clock 3)


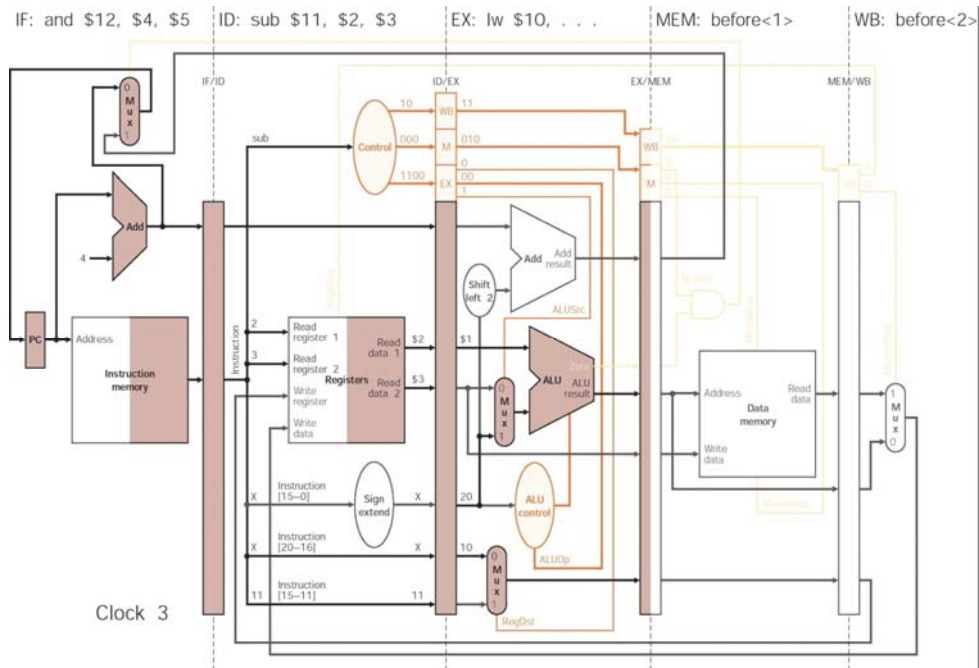


CE, KWU Prof. S.W. LEE 9


Execution Example (Clock 4)

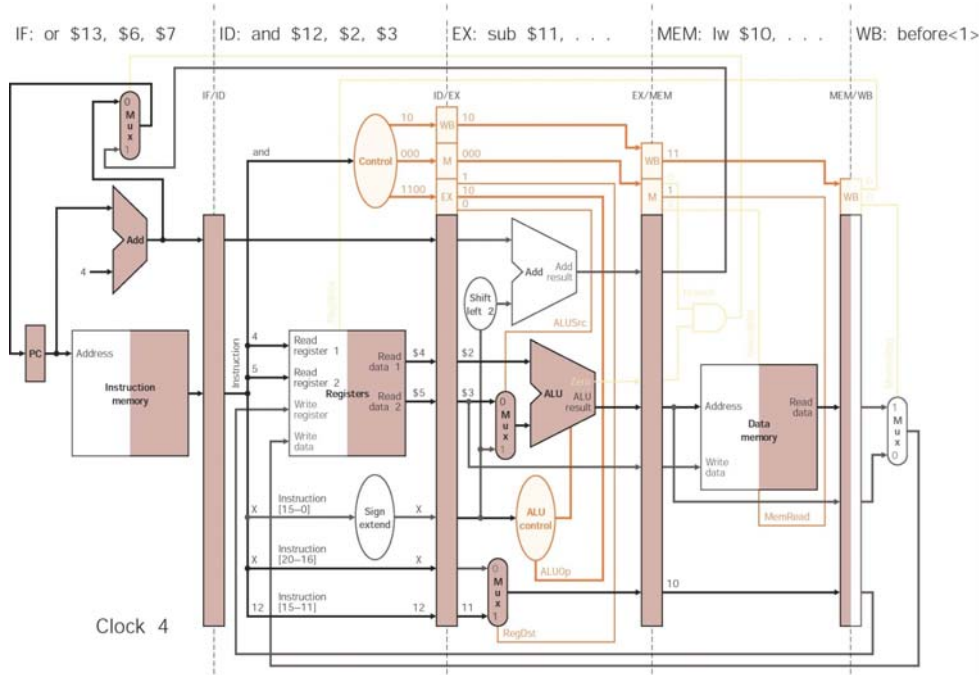

CE, KWU Prof. S.W. LEE 10

  


Execution Example (Clock 7)

 


CE, KWU Prof. S.W. LEE 13

Execution Example (Clock 8)

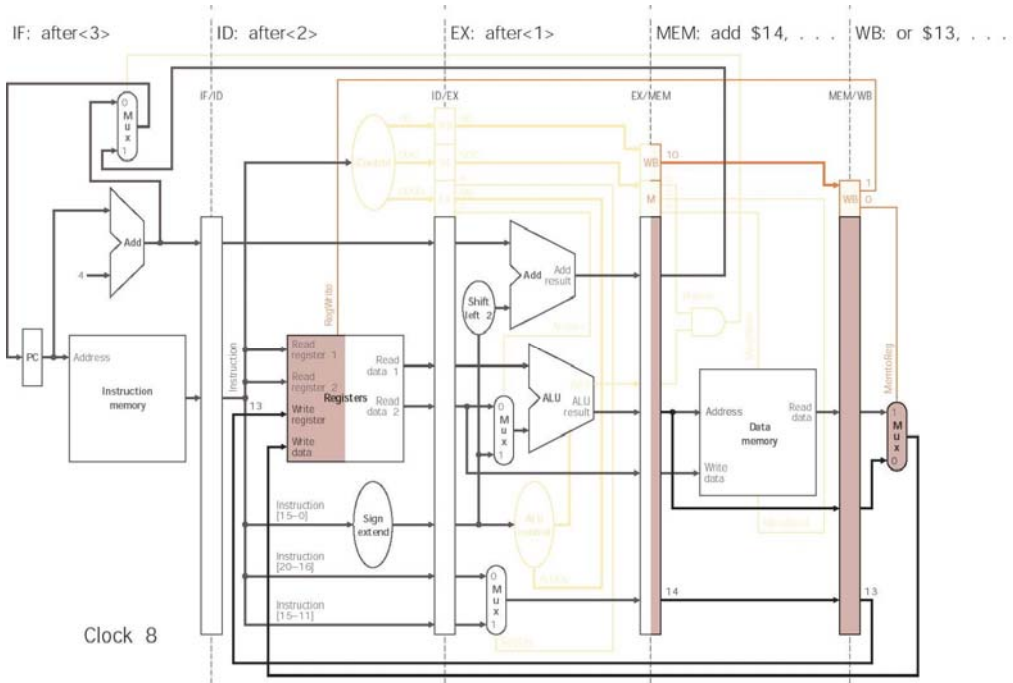



CE, KWU Prof. S.W. LEE 14

Execution Example (Clock 9)

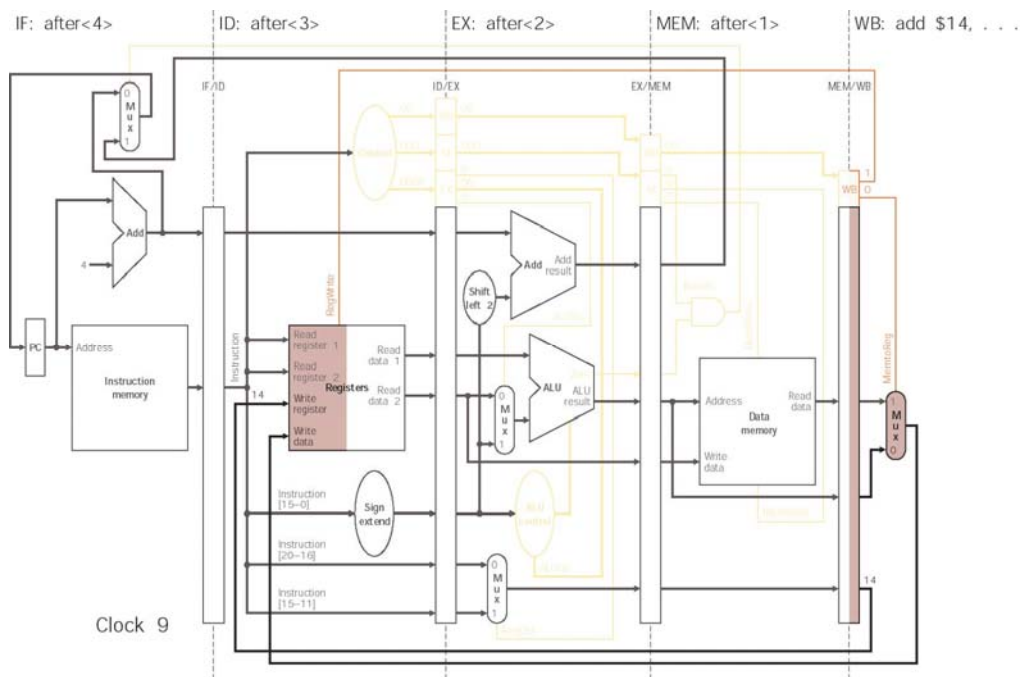

CE, KWU Prof. S.W. LEE 15


Pipeline Hazards Again

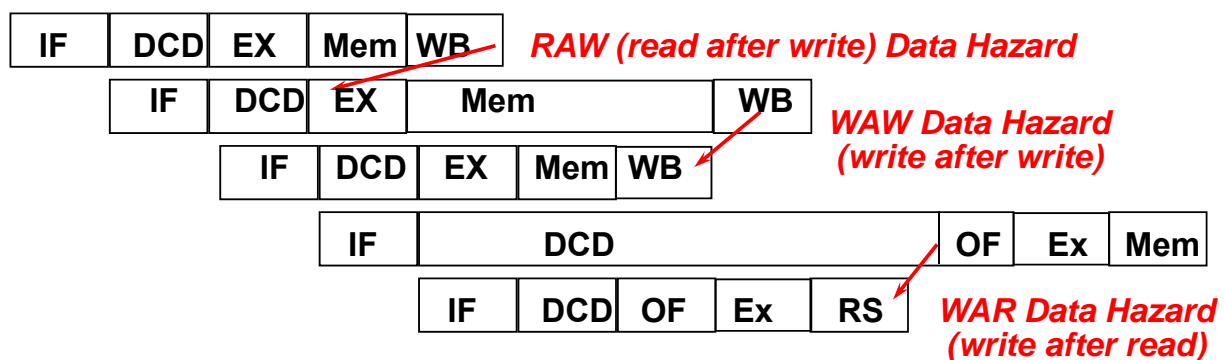 

CE, KWU Prof. S.W. LEE 16


Data Hazards

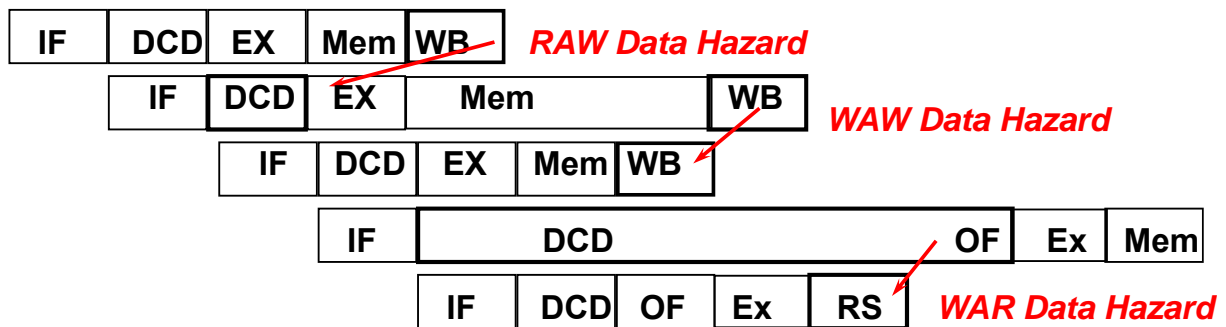- Avoid some “by design”
 - eliminate WAR by always fetching operands early (DCD) in pipe
 - eliminate WAW by doing all WBs in order (last stage, static)
- Detect and resolve remaining ones
 - stall or forward (if possible)



Dependencies

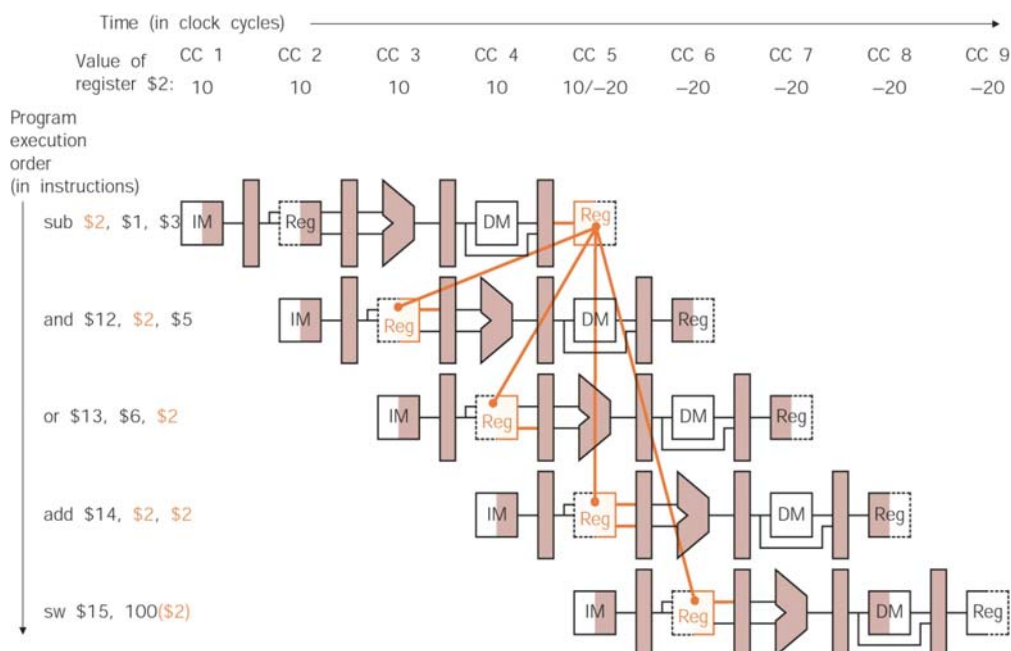- Problem with starting next instruction before first is finished
 - dependencies that “go backward in time” are data hazards



Software Solution

- Have compiler guarantee no hazards
- Where do we insert the “nops” ?


```
sub    $2, $1, $3
and    $12, $2, $5
or     $13, $6, $2
add    $14, $2, $2
sw     $15, 100($2)
```

nop
nop
nop

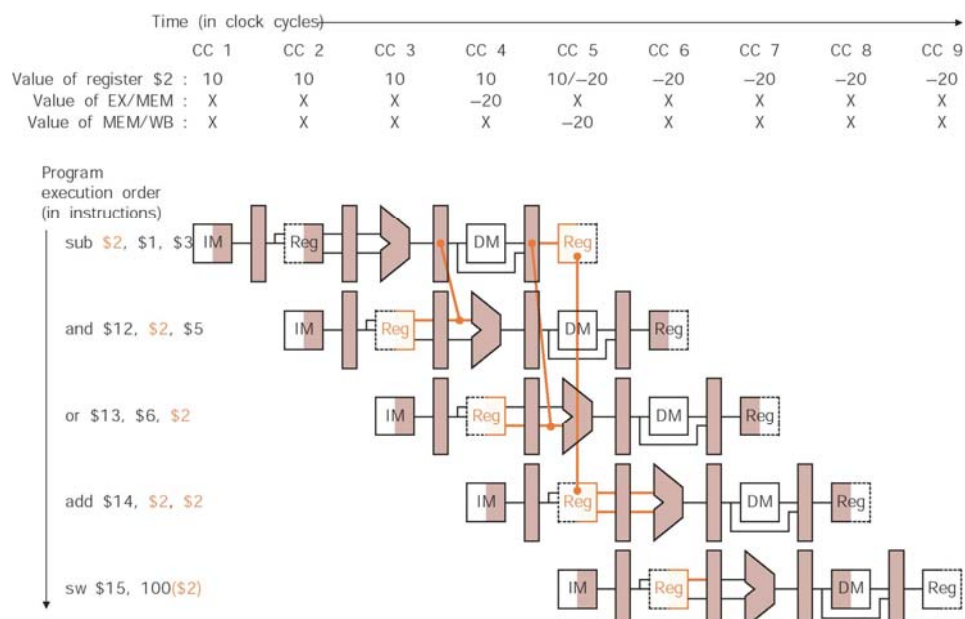
- Problem: this really slows us down!

Forwarding


- Use temporary results, don't wait for them to be written
 - register file forwarding to handle read/write to same register
 - ALU forwarding



Extra hardware for Forwarding

 

a. No forwarding

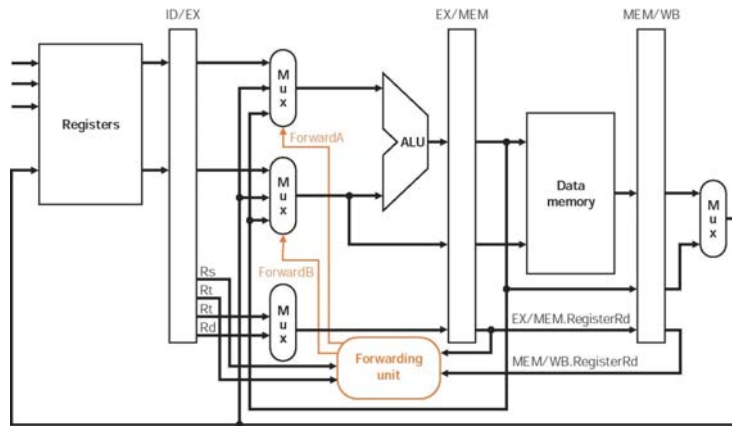

b. With forwarding

CE, KWU Prof. S.W. LEE 21

Hazard Detection

- Suppose instruction i is about to be issued and a predecessor instruction j is in the instruction pipeline.
- A RAW hazard exists on register r if $r \in Rregs(i) \cap Wregs(j)$
 - Keep a record of pending writes (for inst's in the pipe) and compare with operand regs of current instruction.
 - When instruction issues, reserve its result register.
 - When on operation completes, remove its write reservation.
- A WAW hazard exists on register r if $r \in Wregs(i) \cap Wregs(j)$
- A WAR hazard exists on register r if $r \in Wregs(i) \cap Rregs(j)$

Detecting the Need to Forward

- Pass register numbers along pipeline
 - e.g., ID/EX.RegisterRs = register number for Rs sitting in ID/EX pipeline register
 - ALU operand register numbers in EX stage are given by
 - ID/EX.RegisterRs, ID/EX.RegisterRt
 - Data hazards when
 - 1a. EX/MEM.RegisterRd = ID/EX.RegisterRs
 - 1b. EX/MEM.RegisterRd = ID/EX.RegisterRt
 - 2a. MEM/WB.RegisterRd = ID/EX.RegisterRs
 - 2b. MEM/WB.RegisterRd = ID/EX.RegisterRt
- }

}

}

}

Fwd from
EX/MEM
pipeline reg

Fwd from
MEM/WB
pipeline reg

 - But only if forwarding instruction will write to a register!
 - EX/MEM.RegWrite, MEM/WB.RegWrite
 - And only if Rd for that instruction is not \$zero (for MIPS)
 - EX/MEM.RegisterRd \neq 0,
MEM/WB.RegisterRd \neq 0
- CE, KWU Prof. S.W. LEE 23
- ## Forwarding Conditions

- EX hazard
 - if (EX/MEM.RegWrite and (EX/MEM.RegisterRd \neq 0)
and (EX/MEM.RegisterRd = ID/EX.RegisterRs))
ForwardA = 10
 - if (EX/MEM.RegWrite and (EX/MEM.RegisterRd \neq 0)
and (EX/MEM.RegisterRd = ID/EX.RegisterRt))
ForwardB = 10
 - MEM hazard
 - if (MEM/WB.RegWrite and (MEM/WB.RegisterRd \neq 0)
and (MEM/WB.RegisterRd = ID/EX.RegisterRs))
ForwardA = 01
 - if (MEM/WB.RegWrite and (MEM/WB.RegisterRd \neq 0)
and (MEM/WB.RegisterRd = ID/EX.RegisterRt))
ForwardB = 01
- CE, KWU Prof. S.W. LEE 24


Double Data Hazard

- Consider the sequence:
 - add \$1,\$1,\$2
 - add \$1,\$1,\$3
 - add \$1,\$1,\$4
- Both hazards occur
 - Want to use the most recent
- Revise MEM hazard condition
 - Only fwd if EX hazard condition isn't true

Revised Forwarding Condition


- MEM hazard
 - if (MEM/WB.RegWrite and (MEM/WB.RegisterRd \neq 0)
and not (EX/MEM.RegWrite and (EX/MEM.RegisterRd \neq 0)
and (EX/MEM.RegisterRd = ID/EX.RegisterRs))
and (MEM/WB.RegisterRd = ID/EX.RegisterRs))
ForwardA = 01
 - if (MEM/WB.RegWrite and (MEM/WB.RegisterRd \neq 0)
and not (EX/MEM.RegWrite and (EX/MEM.RegisterRd \neq 0)
and (EX/MEM.RegisterRd = ID/EX.RegisterRt))
and (MEM/WB.RegisterRd = ID/EX.RegisterRt))
ForwardB = 01

Datapath supporting Forwarding

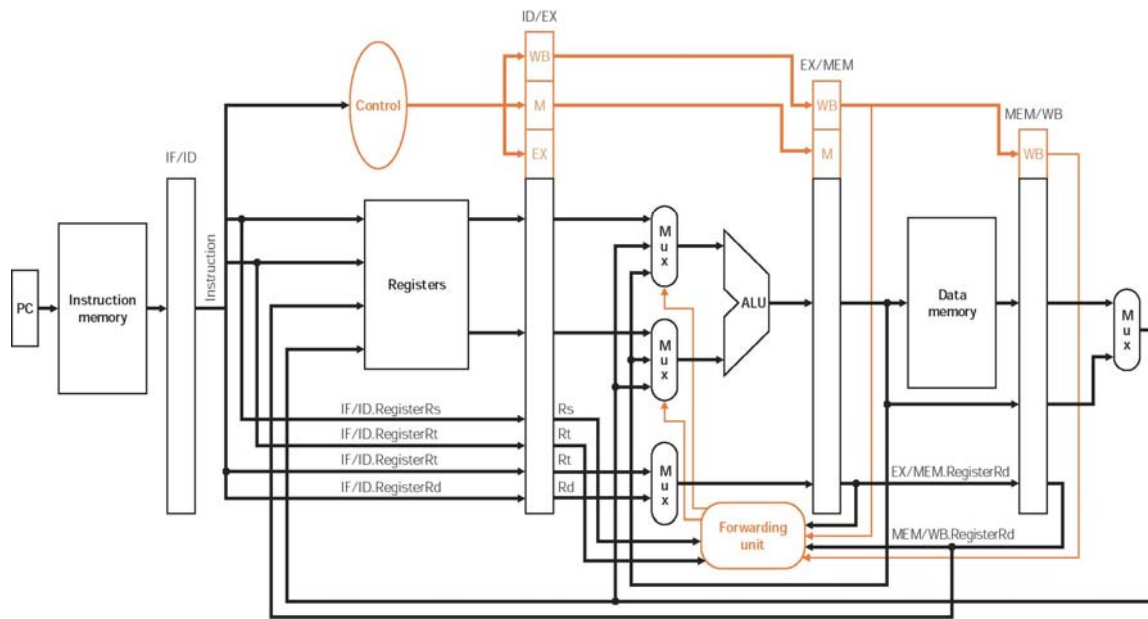


CE, KWU Prof. S.W. LEE 27

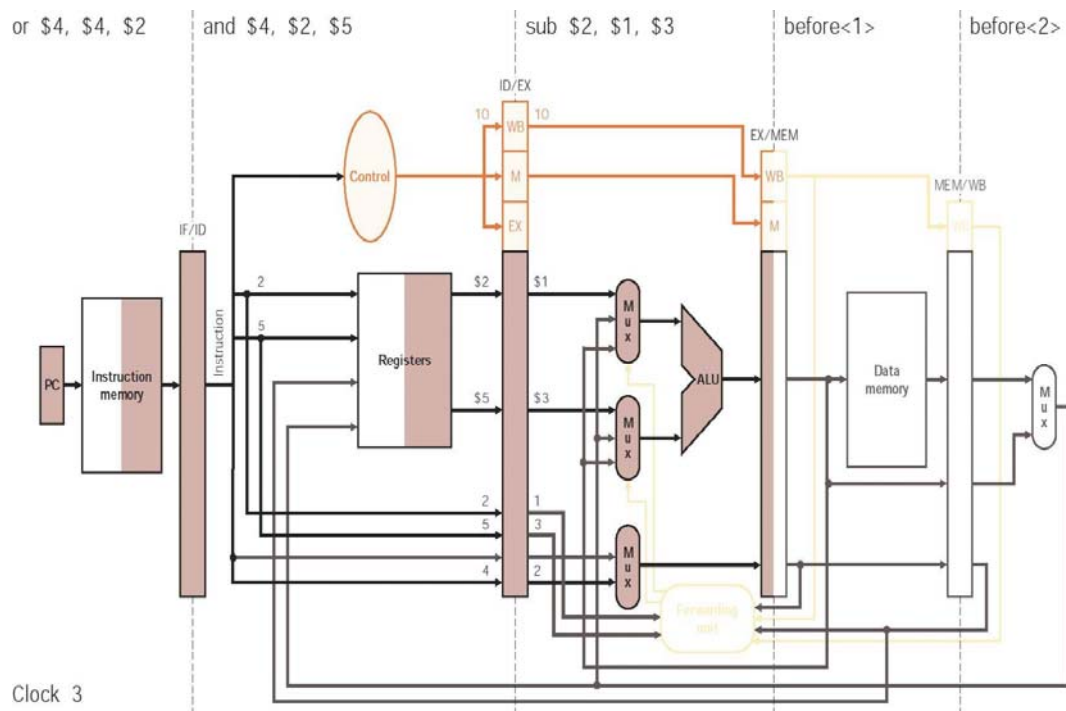Modified Execution Example with Forwarding (C3)




CE, KWU Prof. S.W. LEE 28

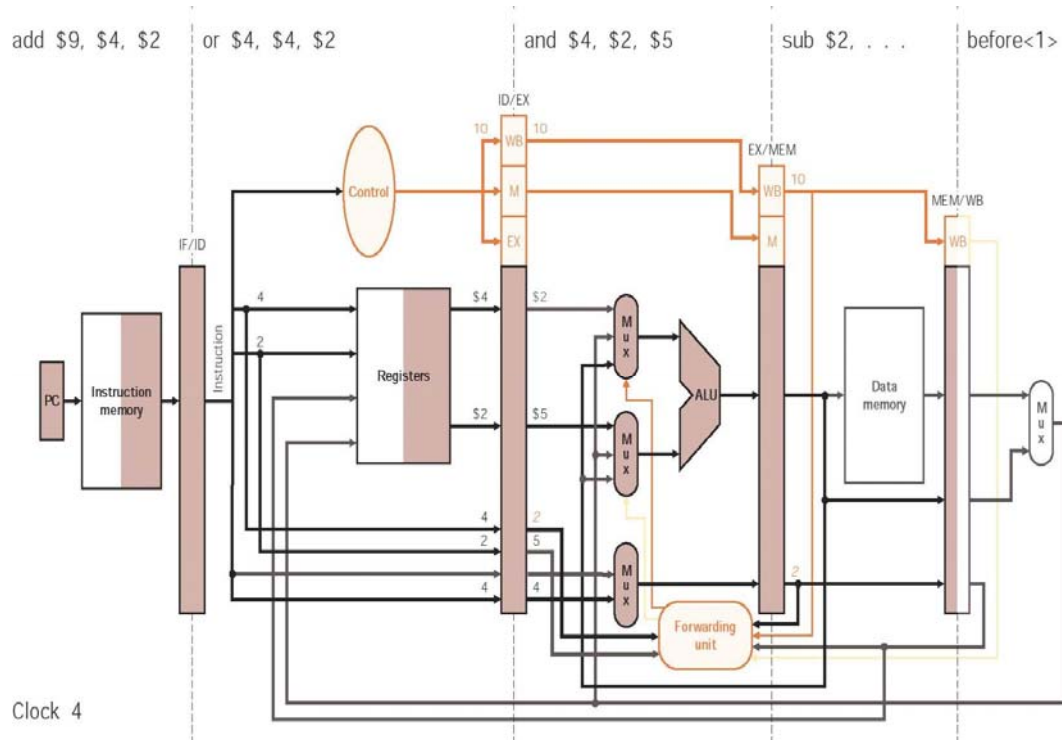Modified Execution Example with Forwarding (C4)




CE, KWU Prof. S.W. LEE 29

 Modified Execution Example with Forwarding (C5)




CE, KWU Prof. S.W. LEE 30

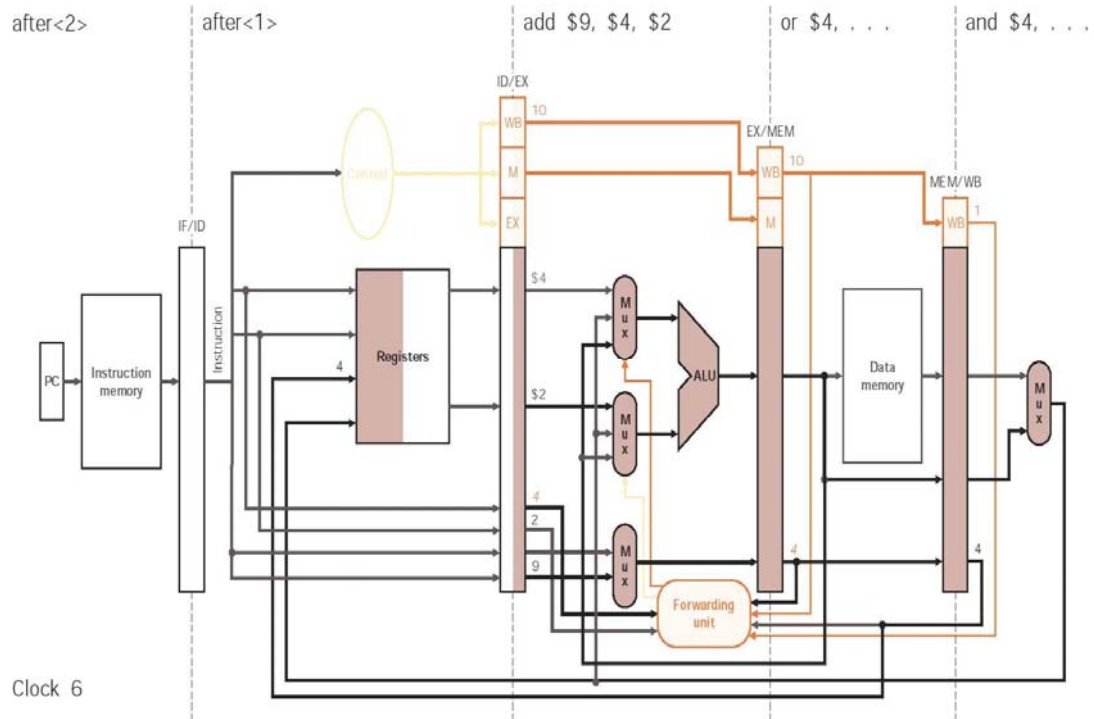Modified Execution Example with Forwarding (C6)



CE, KWU Prof. S.W. LEE 31

Added MUX for selecting ALU Src B

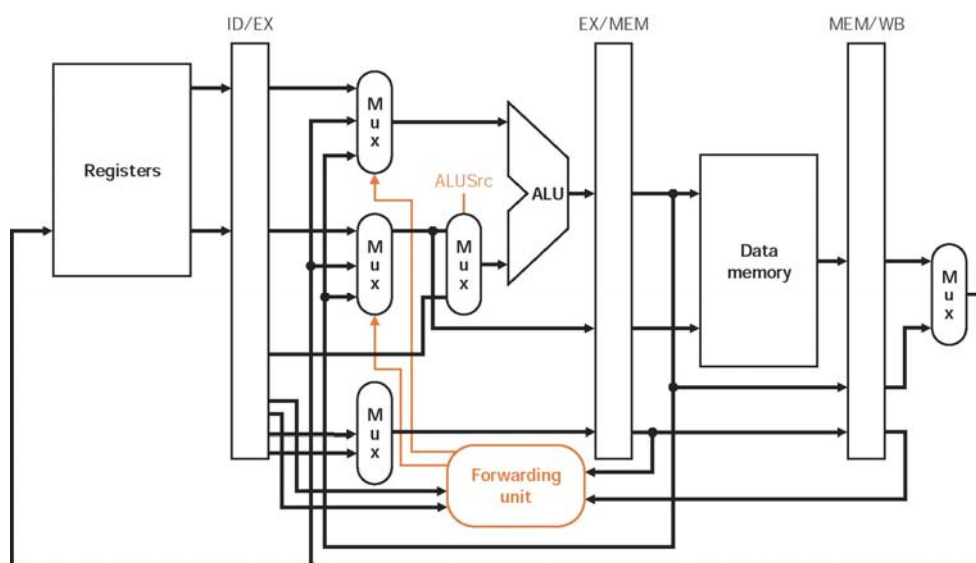


- For signed immediate

CE, KWU Prof. S.W. LEE 32

Can't always forward

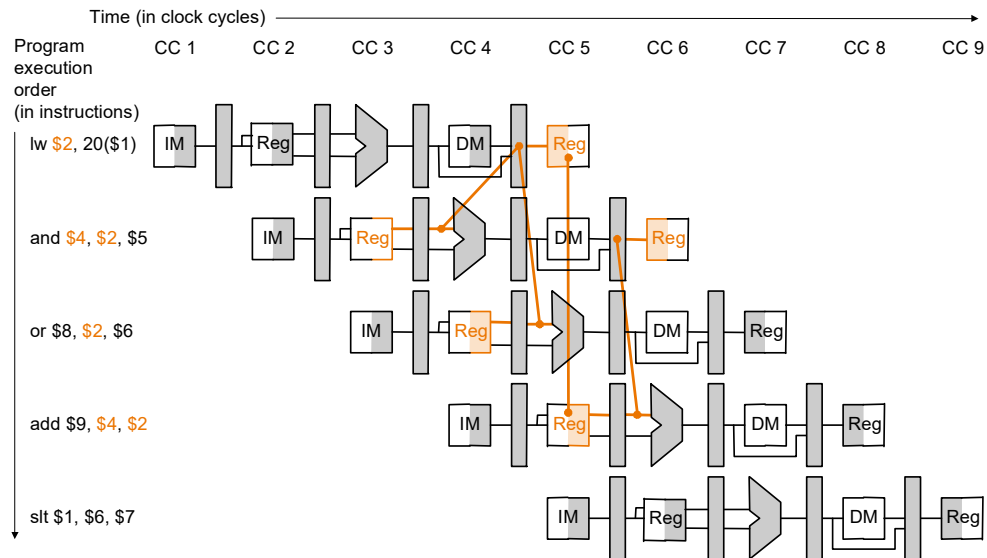
- Load word can still cause a hazard:
 - an instruction tries to read a register following a load instruction that writes to the same register.



- Thus, we need a hazard detection unit to “stall” the load instruction

Stalling

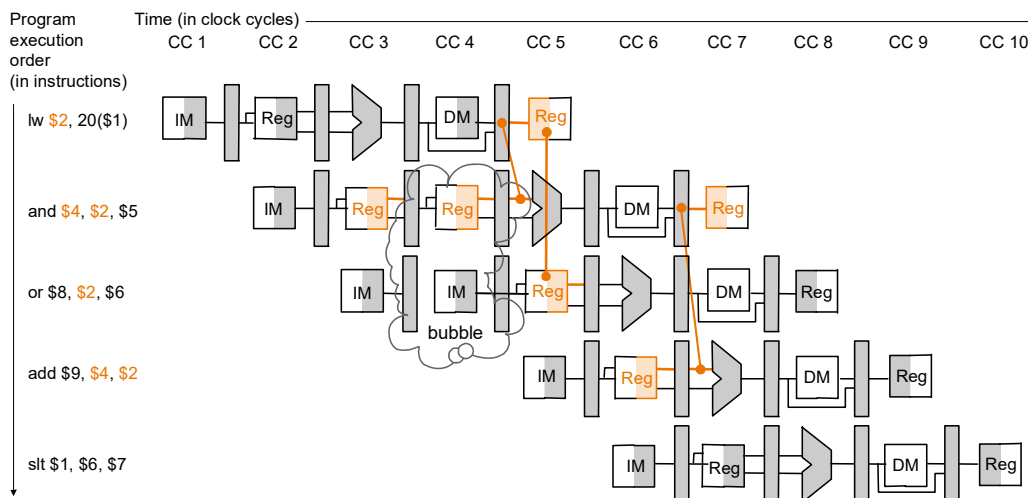- We can stall the pipeline by keeping an instruction in the same stage



Load-Use Hazard Detection

- Check when using instruction is decoded in ID stage
- ALU operand register numbers in ID stage are given by
 - IF/ID.RegisterRs, IF/ID.RegisterRt
- Load-use hazard when
 - ID/EX.MemRead and
 - ((ID/EX.RegisterRt = IF/ID.RegisterRs) or
(ID/EX.RegisterRt = IF/ID.RegisterRt))
- If detected, stall and insert bubble